



CSE 4205

Digital Logic Design

Analysis and Design Procedure of Sequential Circuits

Course Teacher: Md. Hamjajul Ashmafee

Lecturer, CSE, IUT

Email: ashmafee@iut-dhaka.edu



Remaining to Add

- For Design and Analysis Procedure
 - Review other books and internet resources
 - Give 2 hours to make it complete and beautiful
- For Pattern/Sequence detector:
 - Review other books and internet resources
 - Draw the figure with Wacom (slide 11)



Analysis Procedure

From book [Page 250]

- Starting with a sequential Circuit
- Deriving its **state table**
 - 2 variants to represent
- Deriving its **state diagram** from the state table
- Deriving its **state equation** from the state table
 - *Final outcome*
 - *Also, need to describe the behavior of the circuit [Preferred]*
- **Summarize** all *generalized steps*



Design Procedure

From book [Page 254]

- Mention all ***Generalized Steps***
- ***Example*** following those steps



Example of Design Procedure

Sequence/Pattern Detector

Sequence/Pattern Detector

- A **sequential circuit** that takes the **input** of **binary bit streams** and generate an **output true** (e.g. logic 1) when the **target sequence** is detected
 - Bit stream (1s and 0s) will be fed/inserted as input to check for particular pattern or sequence
 - As soon as, the target pattern is detected, it will make the output high
- As the output depends on the current state as well as the external input (x), a **Mealy FSM** is considered





Sequence/Pattern Detector: Types

- Types:
 - **Overlapping**
 - The last bit of one sequence becomes the intermediate bit of the next sequence
 - **Non-overlapping**
 - The last bit of one sequence doesn't become the intermediate bit of the next sequence
- They will be clear from the examples

Design A Sequence Detector

- **Steps:**


- Step 1: Develop the state diagram
- Step 2: Perform the state assignment and state reduction
- Step 3: Select the number and type of the flip flop
- Step 4: Derive Circuit Excitation Table
- Step 5: Derive the expressions for input of the flip flops and output(s)
- Step 6: Develop the circuit

Non-overlapping '101' Mealy Sequence Detector

- **Example:**

Input :	0	1	1	0	1	0	1	0	1	1	0	0	1
Output:	0	0	0	0	1	0	0	0	1	0	0	0	0


- **State Diagram:**

 

Non-overlapping '101' Mealy SD...

• State Assignment:

a	00	Nothing detected
b	10	'1' detected
c	01	'10' detected

 

Non-overlapping '101' Mealy SD...

- **Type and number of flip flops:**

- Two D flip flops

- **Circuit Excitation Table:**

Present States		i/p	Next States		Flip Flop Excitations		O/P
Qa	Qb	x	Qa+	Qb+	Da	Db	y
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	1
1	0	0	0	1	0	1	0
1	0	1	1	0	1	0	0
1	1	0	X	X	X	X	X
1	1	1	X	X	X	X	X

Non-overlapping '101' Mealy SD...

- Expression Derivation:

XY \ I	00	01	11	10
0	0	0	X	0
1	1	0	X	1

$$D_a = Qb' \cdot x$$

XY \ I	00	01	11	10
0	0	0	X	1
1	0	0	X	0


$$D_b = Qa \cdot x'$$

XY \ I	00	01	11	10
0	0	0	X	0
1	0	1	X	0

$$y = Qb \cdot x$$

Non-overlapping '101' Mealy SD...

- Circuit Implementation:**

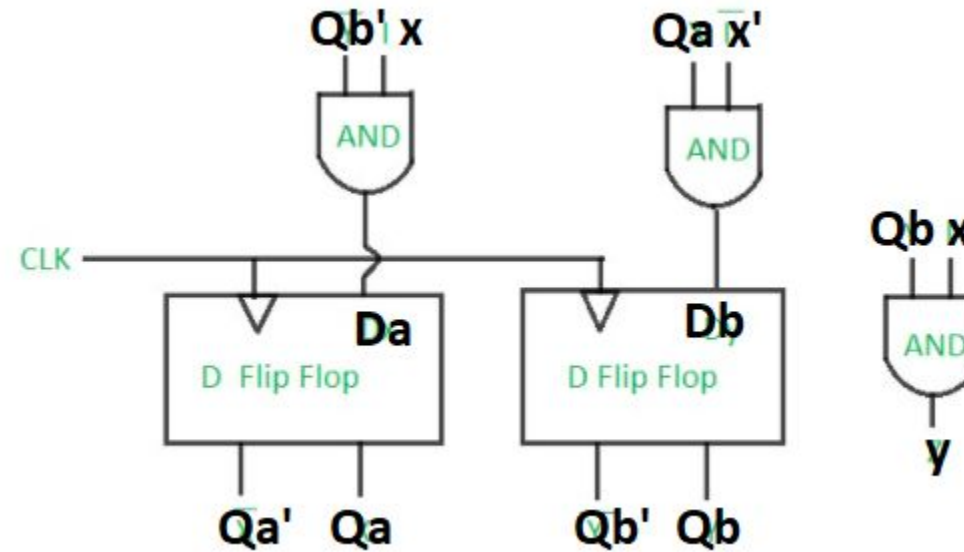


Overlapping 101 Mealy Sequence Detector

- Example:

Input :	0	1	1	0	1	0	1	0	1	1	0	0	1
Output:	0	0	0	0	1	0	1	0	1	0	0	0	0

- State Diagram:

 



Overlapping 101 Mealy SD...

- Others steps would be same as before.



Administration

- abc



Administration

- abc



Administration

- abc



Administration

- abc



Administration

- abc



Administration

- abc



Administration

- **abc**



Motivation

- abc