



CSE 4205

Digital Logic Design

Sequential Logic


Course Teacher: Md. Hamjajul Ashmafee

Lecturer, CSE, IUT

Email: ashmafee@iut-dhaka.edu


Sequential Circuit

- *Combinational circuit + storage elements = Sequential circuit*
- **Storage elements** stores binary information (1 or 0) which are called **states**
 - **This states are time variant**
- *Two possible outcomes of a sequential circuit:*
 - **Present output** of the sequential circuit = F_1 (present input, **present state**)
 - **Next state** of memory element = F_2 (present input, **present state**)
- **Storage element** feeds back its state as **input** to the combinational circuit through a **feedback path**
 - **This feedback path is called a loop**
- **Example:** Counter, Register

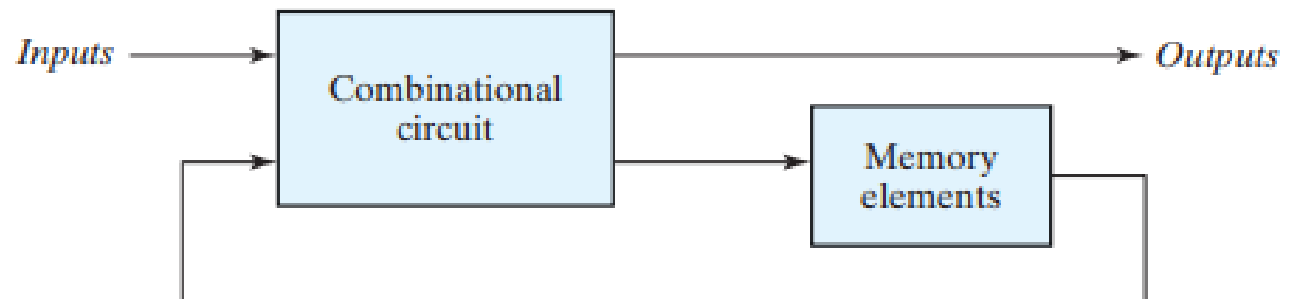

Time Sequence

 - Sequential circuit includes **time sequence** of inputs, outputs and internal memory states
 - This time-sequence determines the **behavior of a sequential circuit**.






Classification of Sequential Circuit

Two types of sequential circuit – based on **timing** of their input signal

 1. Synchronous or clocked sequential circuit
2. Asynchronous or unclocked sequential circuit


Asynchronous Sequential Circuit

- Behavior defined based on the **order/sequence** of input signals at **any instant** of time
 - Only affected whenever the inputs change
 - **No synchronization** with clock pulse
 - Sometimes, activated with **enable input**
- **Example:** Latch




Synchronous Sequential Circuit

 - Behavior defined based on the input signals at **discrete** instants of time
- **Example:** Flip-flop



Clocked Sequential Circuit

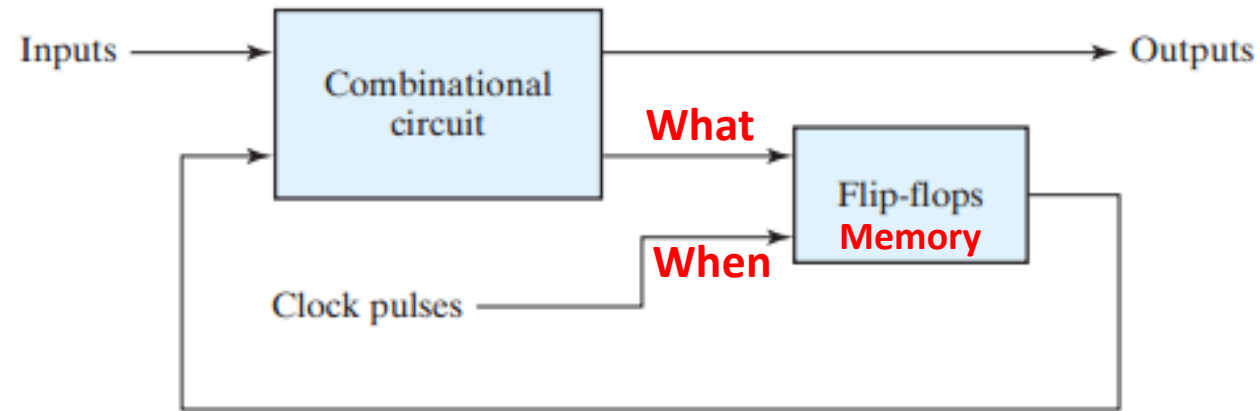


(a) Block diagram




(b) Timing diagram of clock pulses

Clock

 

 Duty Cycle = ratio of the Pulse Width to the Period



T_w = pulse duration




Flip-flops

- **Memory elements** in clocked sequential circuit
- A binary/digital memory cell that stores one bit of information
- **Number of inputs** – **One or more**
- **Two outputs** – **normal (Q)** and **complement (Q')** value of the bit stored
- Also known as a **bistable multivibrator**

Latch

 - Another variant of **memory element**
 - **Propagation delay** is used in this regard
- It has two stable states
- Used to store binary information
 - Binary memory element






Types of Flip-flops

- Based on how the inputs and clock pulses cause transition between two states:
 1. **S-R** (Set-Reset) flip-flop
 2. **D** (Data) flip-flop
 3. **J-K** (J: set, K: reset) flip-flop
 4. **T** (Toggle) flip-flop

S-R (Set-Reset) flip-flop


 
- Two inputs – Set (S) and Reset (R)
- Two outputs – Q and Q' (complement to each other)
- Made of **cross-coupled connection** from output to input constituting a **feedback path**



<i>Inputs</i>		<i>Output</i>
S_n	R_n	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	–

Clocked S-R Flip-Flop

  - **Synchronous circuit**
 - Activated during a clock pulse is present
- From a latch, a **flip-flop** can be produced including **an additional input** to control the behavior of the circuit



Characteristic Table and Truth Table

- **Characteristic table** and **truth table**:
 - **Truth table** with **present input(s)** and **present state(s)** as input column and **next state(s)** as output column refers to a **characteristic table**
 - It refers to the **operational characteristics** of the flip-flop

S-R Flip-Flop - Characteristic table

- **Characteristic table** and **Characteristic equation** of S-R flip flop

<i>Flip-flop inputs</i>		<i>Present output</i>	<i>Next output</i>
<i>S</i>	<i>R</i>	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

$$Q_{n+1} = S + R'Q_n$$



$$SR = 0.$$



Preset and Clear Inputs

- Initially (at t_0), a circuit is **uncertain** with Q and Q' states
- They should be assigned with either **set** or **reset** state with direct or asynchronous inputs
 - Also, called as **overriding** inputs
 - These inputs are individually named as **preset (Pr)** and **clear (Cr)**
- These inputs are not synchronized with clock
 - They can be applied at any time
 - **CLK = 0 or 1, doesn't care at all [but, preferred to be applied when clock is inactive]**
- **Pr = 0** and **Cr = 0** must not be applied, as it leads to an uncertain state
- **Pr** and **Cr** inputs are used with bubbles considering them **active low**

Preset and Clear Inputs...

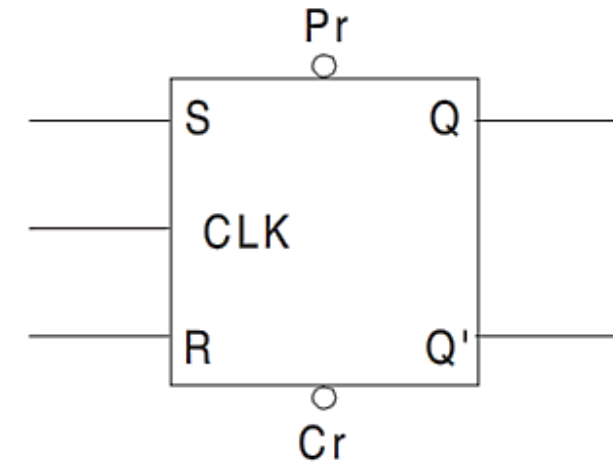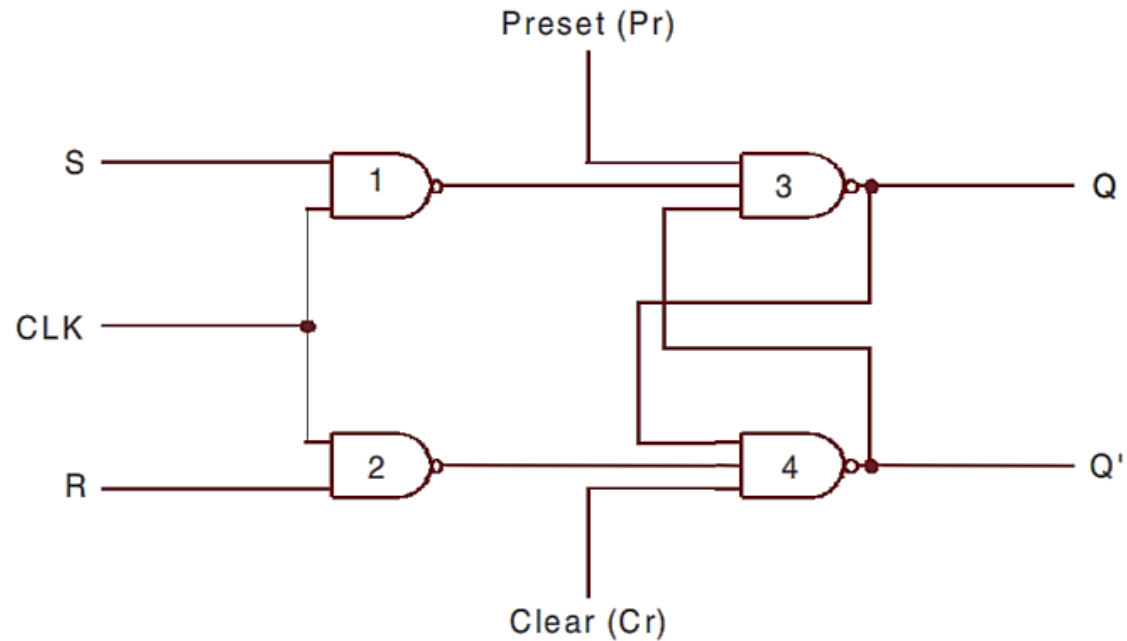

Preset and Clear Inputs...

<i>Inputs</i>		<i>Output</i> <i>Q</i>	<i>Operation performed</i>
<i>Cr</i>	<i>Pr</i>		
1	1	Based on inputs	Normal flip-flop
1	0	1	Preset
0	1	0	Clear
0	0	—	Uncertain



D Flip-Flop

- Derivation from S-R flip-flop
- **Truth table** and **all cases** of D flip-flop
- **Block diagram** of D flip-flop
- D flip-flop with ***Pr*** and ***Cr*** inputs
- **Characteristic table** and **equation** of D flip-flop
- **Application – register**




J-K Flip-Flop

- Very similar to an S-R flip-flop
 - **J and K** behave like inputs **S and R** to set and reset the flip-flop
- **Advantage: Eliminates** the **undefined condition** of an S-R flip-flop
 - Only difference between S-R and J-K flip-flop
 - When $J=K=1$, the flip-flop is said to be in a ***toggle state***
 - ***Toggling*** means complementing the state in each clock pulse



J-K Flip-Flop – Implementation

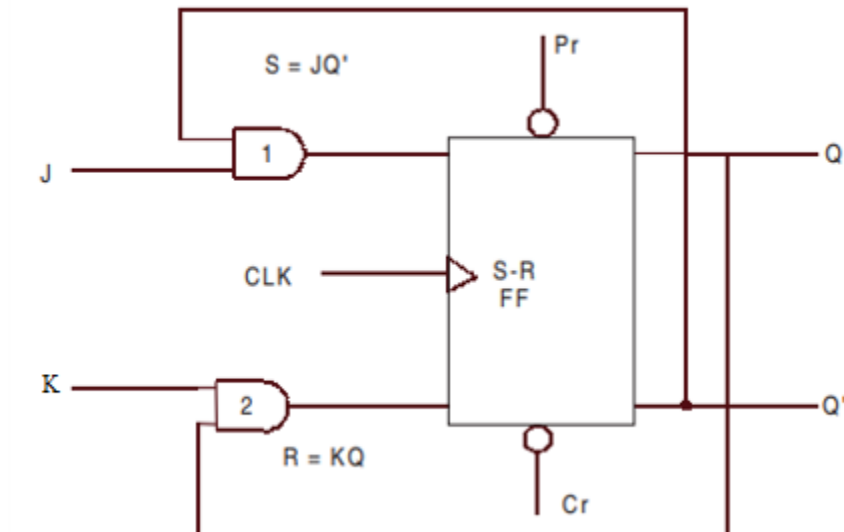- Implementation **from S-R flip flop**
 - Another **level of feedback** path is included
 - Inputs **J and K** of J-K flip-flop are ANDed (**cross-coupled**) with **Q'** and **Q** respectively to obtain the inputs, S and R for S-R flip-flop



J-K Flip-Flop – Implementation...

  - Circuit diagram and block diagram of a J-K flip flop with NAND gates



J-K Flip-Flop – Truth Table

<i>Inputs</i>		<i>Output</i>
J_n	K_n	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	Q'_n




J-K Flip-Flop – Characteristic Table

- Characteristic table and characteristic equation for J-K flip-flop

J-K Flip-Flop – Race Around Condition

- Assumption for basic J-K flip-flop:
 - The inputs will not be changed any more during a clock pulse
 - But, it is not true because of the feedback connections
- Consider the scenario: **J=K=1**
 - If $Q=1$, after Δt time, it will be $Q=0$
 - Next, if $Q=0$, after another Δt time, it will be $Q=1$
- So, basically, during t_p time, the output Q will oscillate between 0 and 1 after each Δt time
- And, after t_p time, the output Q is **not certain**.
- This situation is called “**Race-Around Condition**”

 

Δt = propagation delay
 t_p = pulse duration
Level triggered clock pulse




Race Around Condition – Solutions

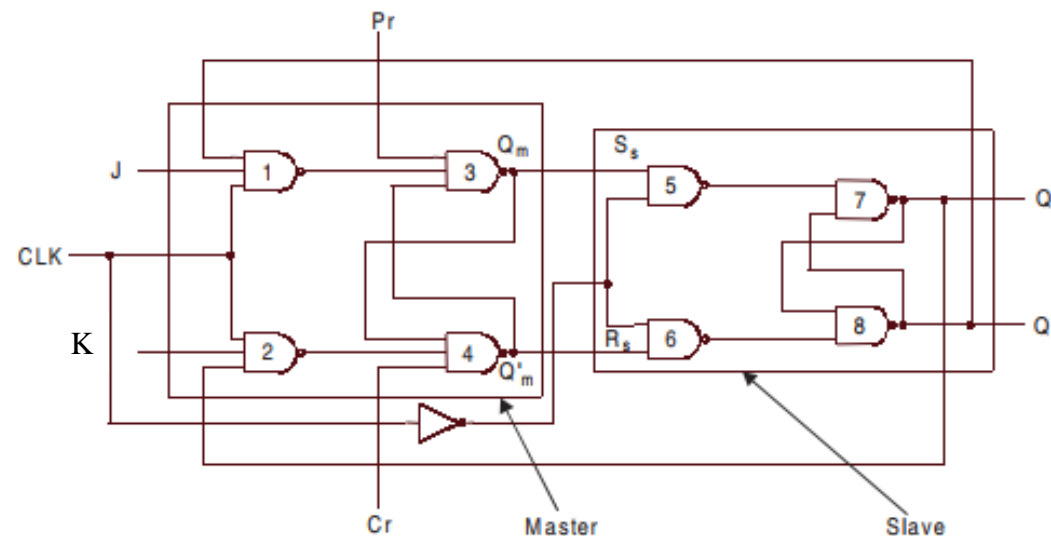1. If Δt is in nanoseconds and t_p in microseconds, output will be changed thousands of times within a clock pulse
2. Master-Slave (M-S) flip-flop
3. Edge triggered flip-flop

Race Around Condition – Master-Slave J-K Flip-Flop

- A system of two **cascaded** flip-flops – master and slave flip-flops
- A **clock pulse** is applied to **master** and the **inverted form of the same clock** is applied to the **slave**
- **How to solve RAC problem?**
 - When $CLK=1$, gates 5 and 6 will not respond. Output Q and Q' will only change when $CLK=0$.





T Flip-Flop

- A slight modification of the J-K flip-flop
 - J and K inputs are tied together – **have same input**
 - Referred as **T flip-flop**
 - **It has the ability to toggle**
- One input (**T**) and two outputs **Q** and **Q'**
- Two states – **toggle (T=1)** and **memory (T=0)** states
- **Usage:** Counter, switching circuits



Triggering of Flip-flops

- Level Triggering
- Edge Triggering



Excitation Table

- A **tabulation** to figure out **all possible input conditions** to obtain the **desired output condition**
 - It is required to **design a sequential circuit** when present state and next state of the flip-flop is specified

Excitation Table of all Flip-Flops

<i>Present State (Q_n)</i>	<i>Next State (Q_{n+1})</i>	<i>S-R FF</i>		<i>D-FF</i>	<i>J-K FF</i>		<i>T-FF</i>
		S_n	R_n	D_n	J_n	K_n	T_n
0	0	0	X	0	0	X	0
0	1	1	0	1	1	X	1
1	0	0	1	0	X	1	1
1	1	X	0	1	X	0	0

Interconversion of Flip-flops

- A **conversion logic** is required to be designed for such conversions of flip-flops

