
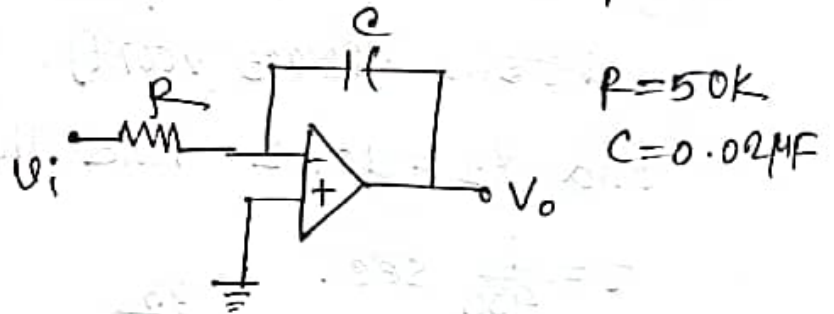


Assignment (15 Marks)


01. Using an ideal op-amp, design a circuit that will take V_1, V_2 and V_3 as inputs and produce the following output:

$$V_{out} = -10V_1 + 5 \frac{dV_2}{dt} + 2 \int V_3 dt$$

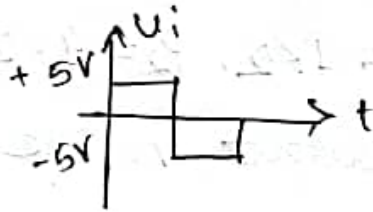
02. A 10 V P-P and 1 kHz rectangular pulse is input, draw the output waveshape for the following circuit:



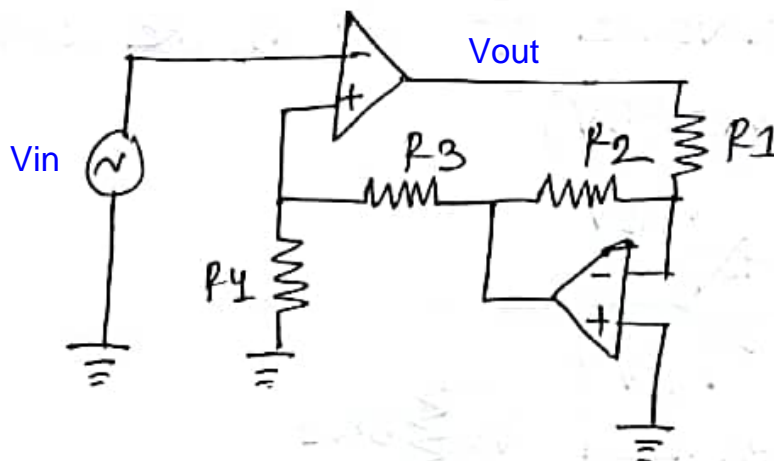
03. Determine the voltage gain of the following op-amp circuit, where $R_1 = R_2 = 15K\Omega$ and $R_3 = R_4 = 5K\Omega$



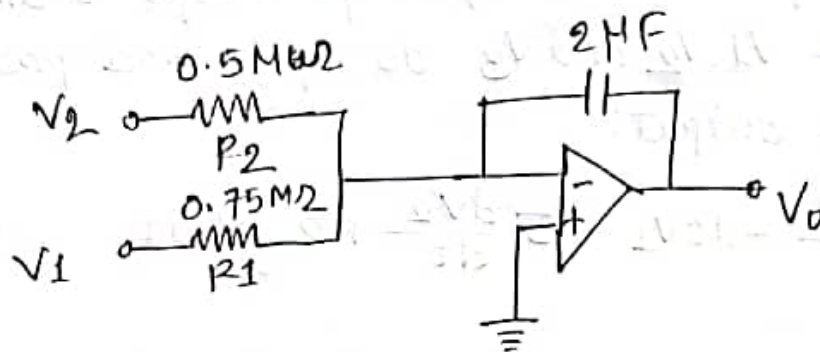
- 04) For the ideal op-amp given below, $V_1 = 10 \sin(200t)$ and $V_2 = 15 \sin(200t)$, find the output voltage, V_o .



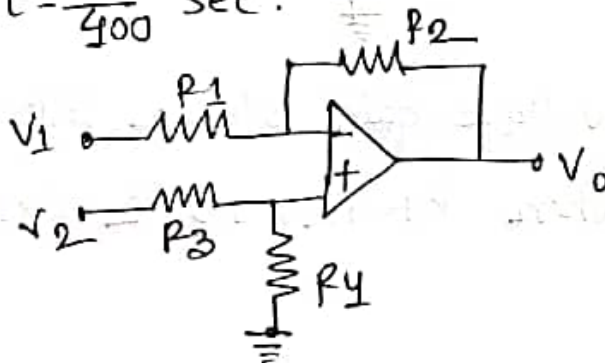
- 05) In the following circuit, $V_1 = 10 \sin(200\pi t)$, $V_2 = 10 \sin 10 \cos(200\pi t)$, $R_1 = 1 \text{ k}\Omega$, $R_2 = 4 \text{ k}\Omega$, $R_3 = 5 \text{ k}\Omega$ and $R_4 = 10 \text{ k}\Omega$. Find the output voltage when $t = \frac{1}{400} \text{ sec}$.



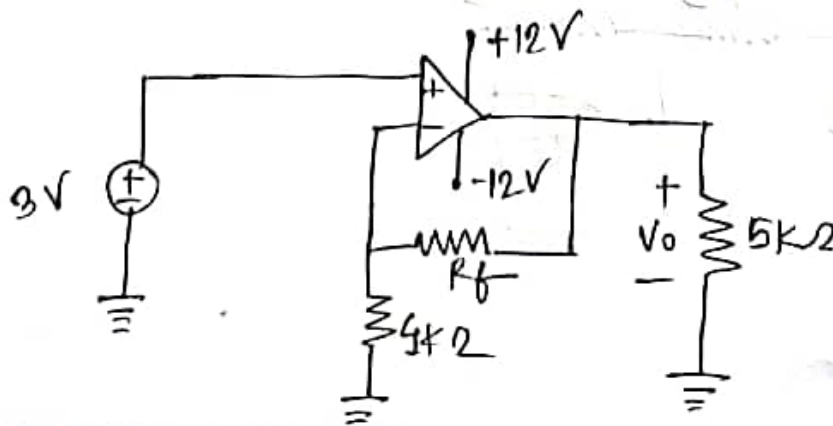
- 06) Find the value of R_f in the following circuit. ($V_o = 75 \text{ V}$)



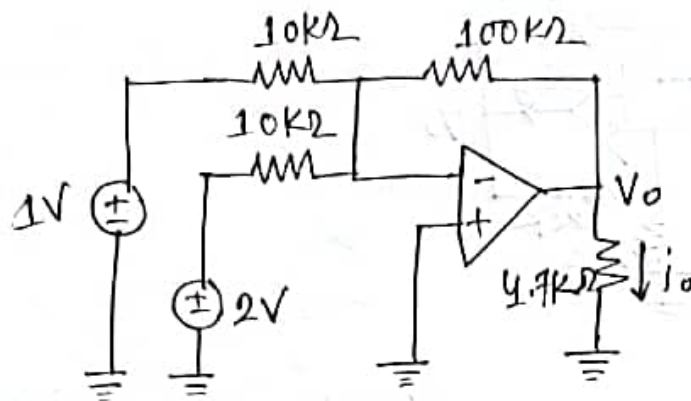
07. Find i_o in the following ideal op-amp.



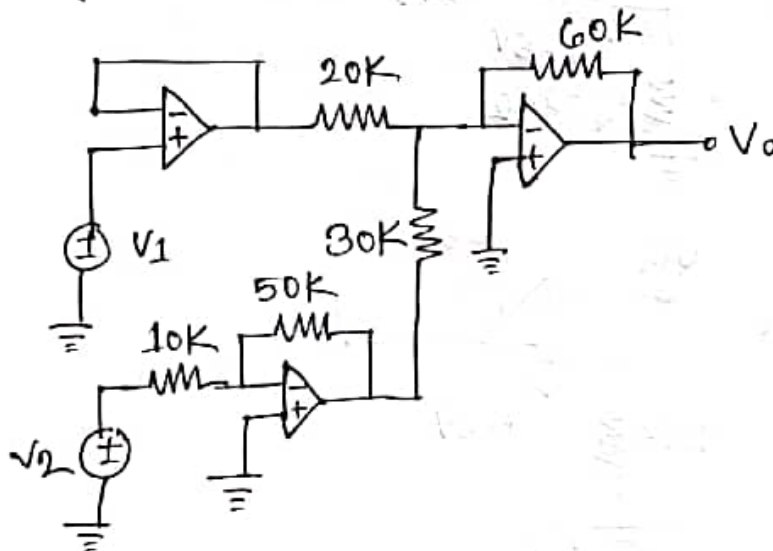
08. Find the output of the op-amp circuit shown in figure below. If $V_1 = 7V$ and $V_2 = 3.1V$





09. Determine the output voltage V_o

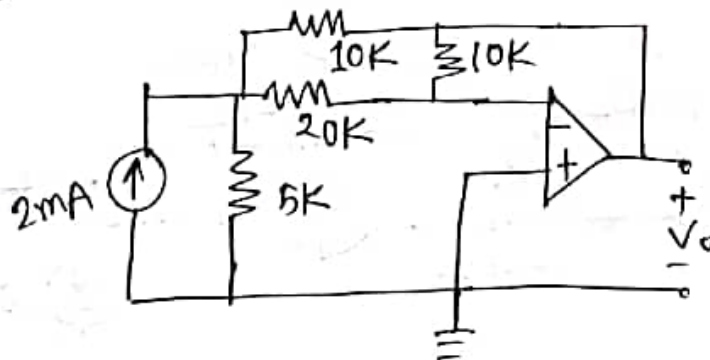

⑩ Find i_x and i_y

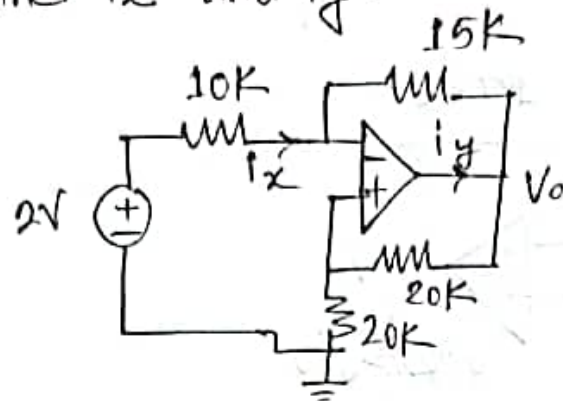

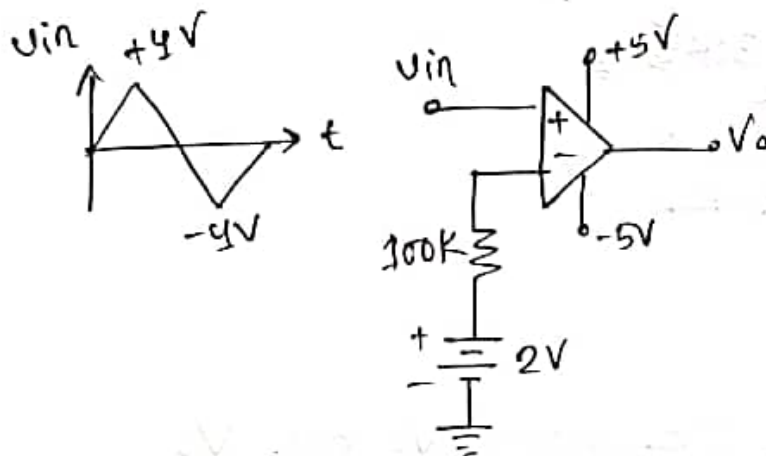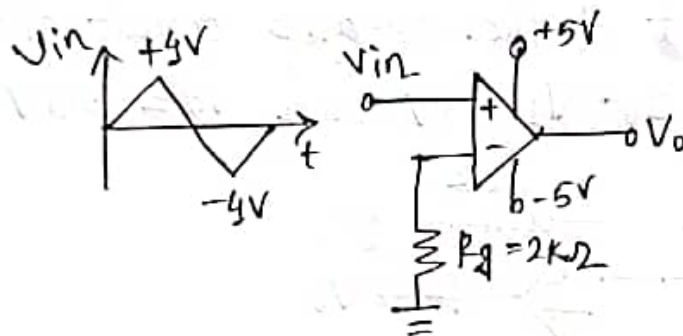⑪. Draw the output shape of the op-amp circuit.



⑫. Find i_o in the op-amp circuit.

