



CSE 4205

Digital Logic Design

ROM, PLA, PAL, ALU

Course Teacher: Md. Hamjajul Ashmafee

AP, CSE, IUT

Email: ashmafee@iut-dhaka.edu




Introduction


- With the advent of **large-scale integration** technology, it is feasible to fabricate large circuits within a single chip
 - A consequence – Programmable Logic Devices (PLD)
 - A kind of LSI
 - A combinational circuit to implement a set of Boolean functions

Concept to Produce PLDs

 
- Normally Boolean functions are expressed by **sum of product** forms or **sum of required minterms**
 - A **decoder** can be used to generate 2^n minterms for n inputs
 - One or more OR gates are required to generate the expected function
- Specially they are used as a **memory device**
 - In spite of being **combinational circuit** devices



General Structure of PLD

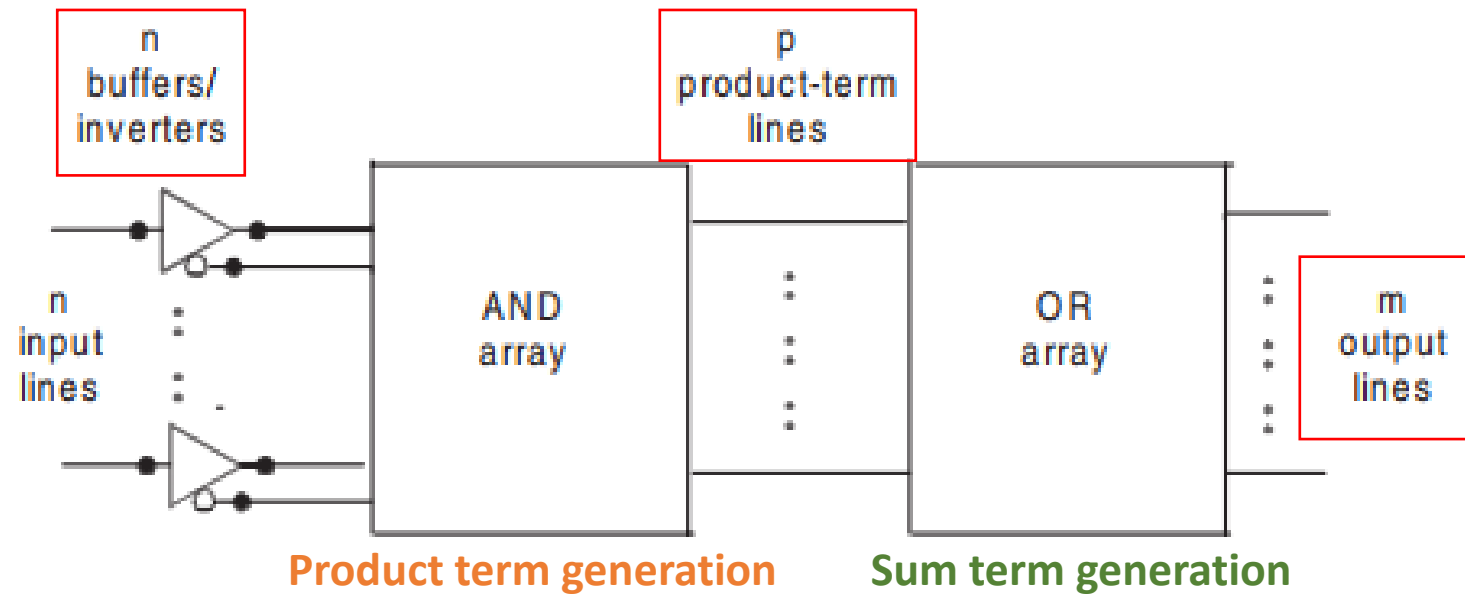

Internal Structure of PLD

 


PLD Classification and Summary

- Read Only Memory (ROM)
- Programmable Logic Array (PLA)
- Programmable Array Logic (PAL)

<i>Device type</i>	<i>AND array</i>	<i>OR array</i>
ROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed



Concept: *Programmable Array*

 - In a **programmable array**, the **connections** of gates are **flexible**
 - To implement a **programmable gate**, a **fuse link** is employed
 - **Example:** a programmable input to an **AND gate**
 - Some of the fuses are blown out (removed/broken) to achieve the desired output of the gate



PLD Notation

  - To simplify the **representation** of PLD connection:
 - A **single line** is drawn into the **logic gate** where the inputs are shown with **perpendicular lines**
 - The connected inputs are indicated by **cross (x)** at the junctions [fusible] and unconnected inputs are left **blanks**
 - Sometimes junctions are presented with **'bold' dots** indicating **permanent junctions**






PLD Types in Details


Read Only Memory (ROM)

- Common Notation – $2^n \times m$ ROM
 - n input lines and m output lines
 - 2^n intermediate ANDed (*i.e.* product/minterm) terms which are **fixed**
 - m outlines lines are **programmable**
 - Also, this notation is considered as **total number of bits** stored as a memory device.
 - 2^n denotes the **total number of addresses**
 - m denotes the **total number of bits per word**
 - A two level logic representation in **sum of minterms** form
 - Block Diagram:

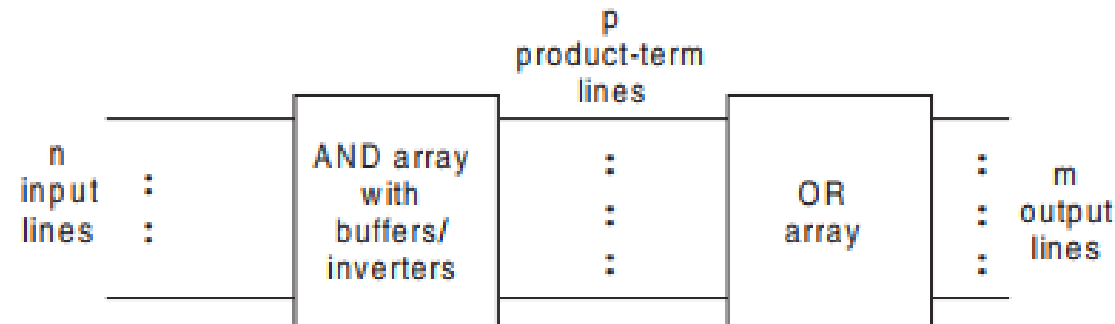


ROM with Decoder

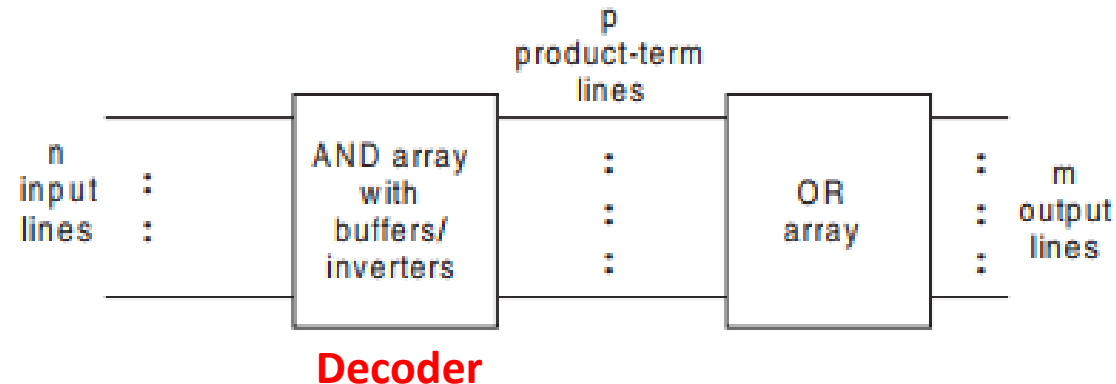
- A **decoder** could be used to implement a **ROM**
 - Each minterm then is applied to required number of **OR gates** using **fusible** links which could be **blown up** selectively as per requirement (shown in logic diagram next)



$2^n \times m$ ROM: *Logic Diagram*

 

$2^n \times m$ ROM: *PLD Notation*

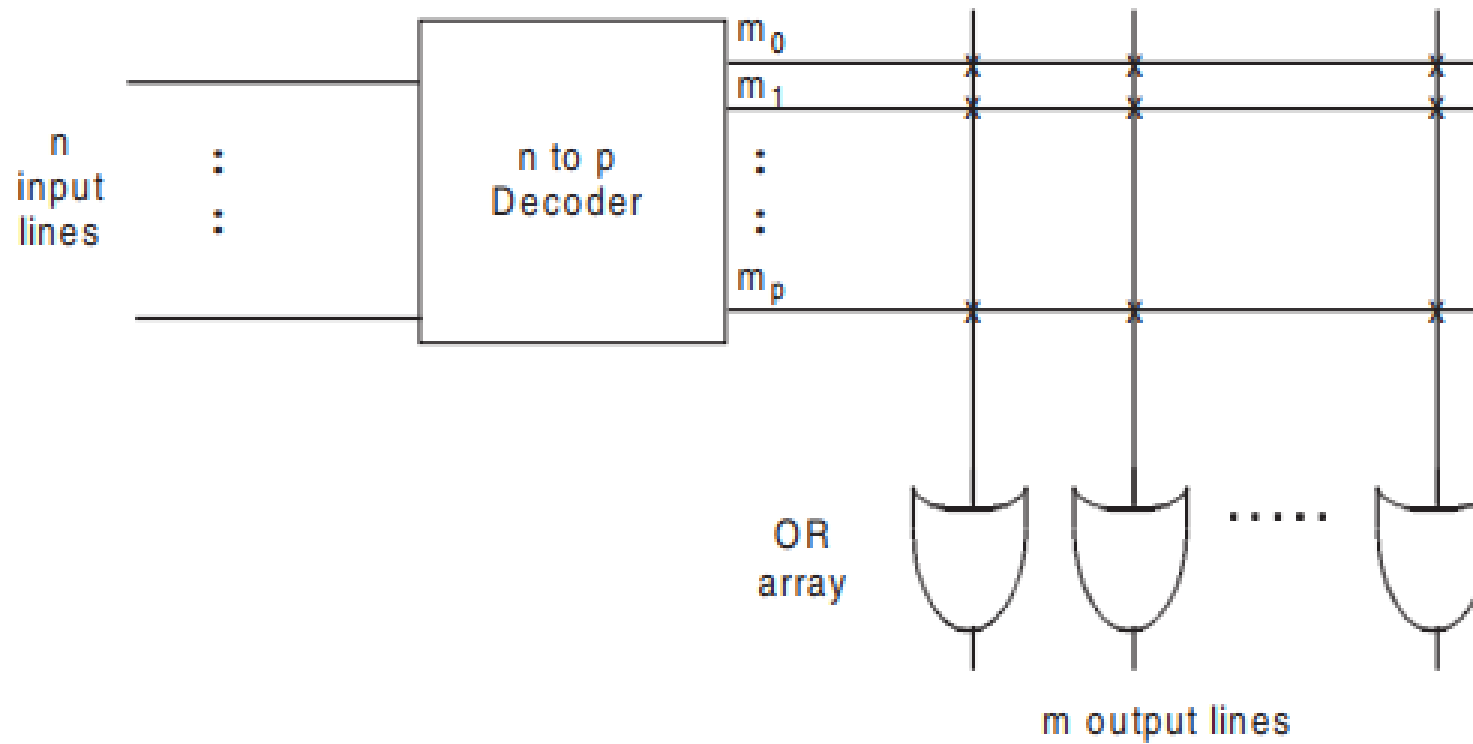



ROM: Example

Too simple to implement with a ROM

$$F_1 (A, B, C) = (0, 1, 2, 5, 7)$$

$$F_2 (A, B, C) = (1, 4, 6).$$


i.e. a **2³x2** or **8x2** ROM is required.

Program table or truth table for ROM:

<i>Decimal Equivalent</i>	<i>Input Variables</i>			<i>Outputs</i>	
	<i>A</i>	<i>B</i>	<i>C</i>	<i>F₁</i>	<i>F₂</i>
0	0	0	0	1	0
1	0	0	1	1	1
2	0	1	0	1	0
3	0	1	1	0	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	0	1
7	1	1	1	1	0


ROM: Example...

- Logic diagram:

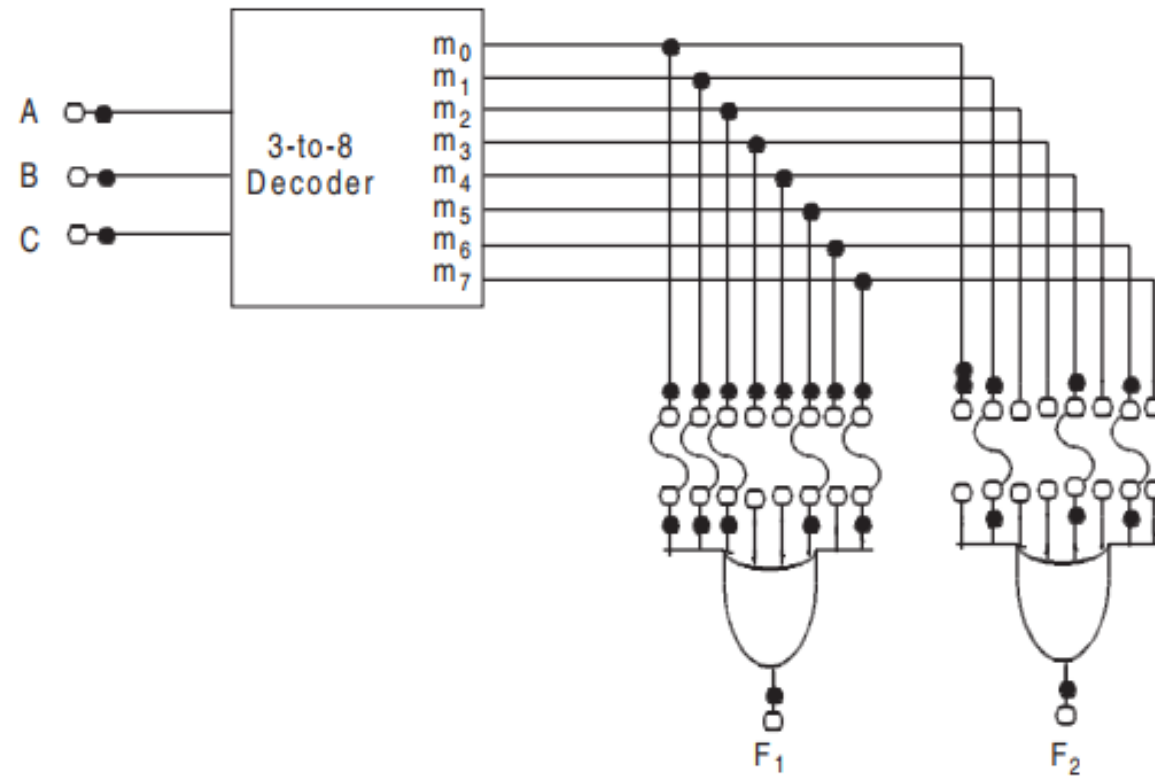


ROM: Example...

- Logic diagram with PLD notation :

 

ROM: Example...

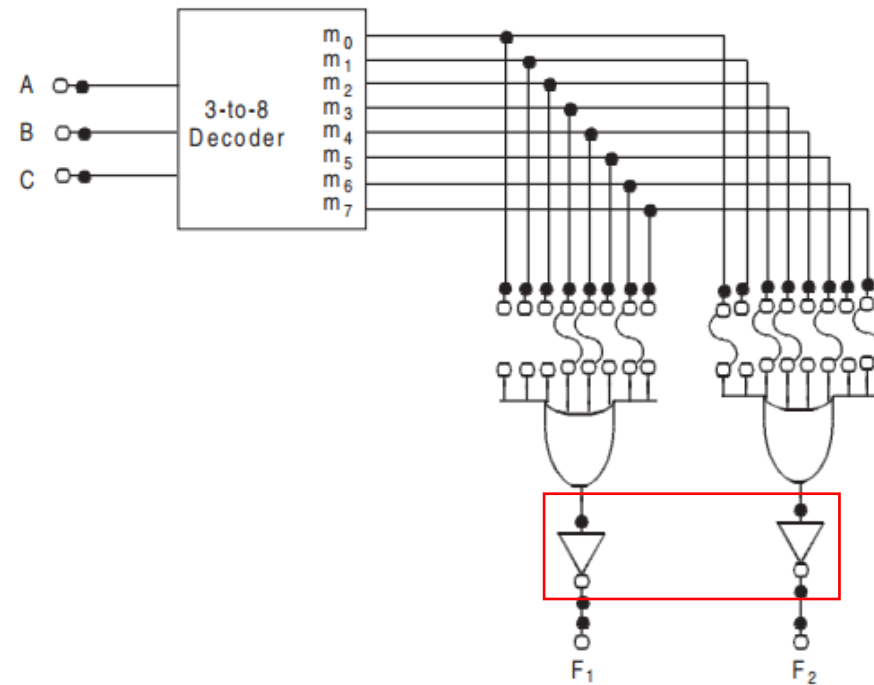- Some ROMs are available with **inverter logic gate (NOT)** with each OR gates



Programmable Logic Array (PLA)

- **Motivation:**


- A combinational circuit may contain **don't care conditions** which will never occur
 - A **waste of memory** considering **don't cares** as valid *minterms*
 - **Example:** Code conversion from BCD to Excess 3 where **6 addresses will not be used** for a 16x4 ROM
 - A waste of **6x4** bit locations
- PLA (kind of LSI) is **more economical** to use where don't care cases are **excessive**




Concept of PLA

- Common notation: **n** x **p** x **m**
 - **n** = number of inputs
 - **p** = number of product terms
 - **m** = number of outputs (or sum terms)
- Total number of **programmable links** = $(2n \times p) + (p \times m) + m$
- The basic difference between ROM and PLA is in the **number of the product term**
 - **i.e.** 2^n (ROM) \gg p (PLA)
 - **e.g.** 16 x **48** x 8 PLA. Here the number of product term is drastically reduced

PLA: Block Diagram

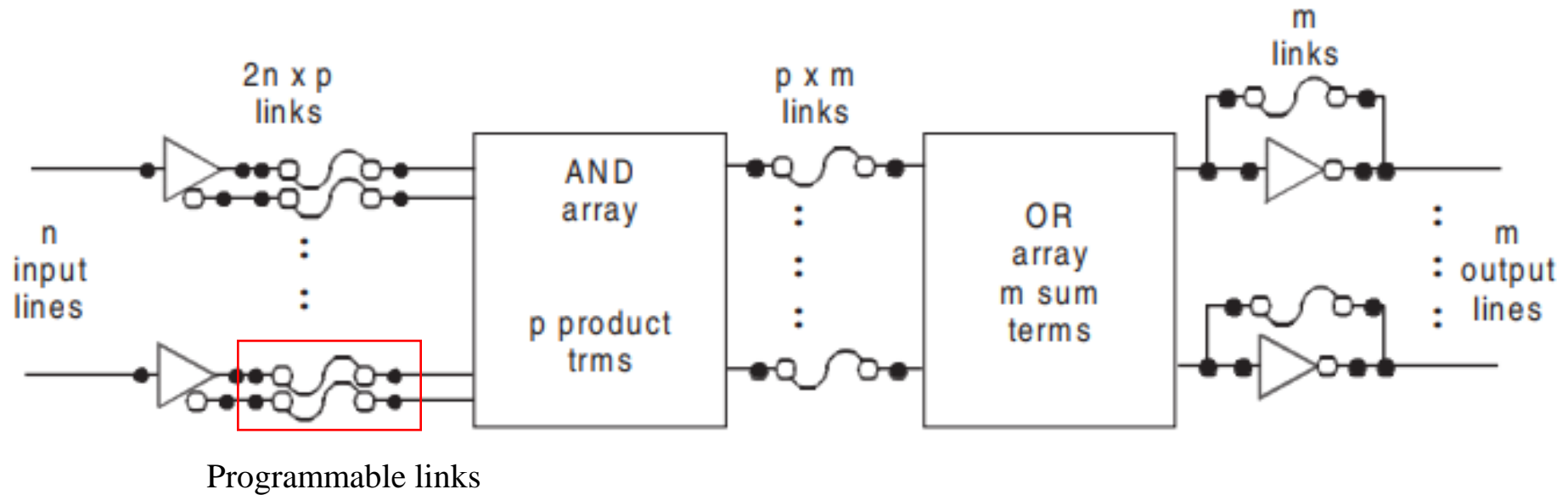

PLA: General Structure or Logic Diagram

 

PLA: Example

Too simple to implement with a PLA

- **Example:** Use a **3 x 4 x 2** PLA to implement the following Boolean expressions

$$F_1 (A, B, C) = (0, 1, 3, 4)$$

$$F_2 (A, B, C) = (1, 2, 3, 4, 5).$$

- To get required and reduced product terms, **simplified expressions** are:

	B'C'	B'C	BC	BC'
A'	1	1	1	
A	1			

$$F_1 = B'C' + A'C$$

	B'C'	B'C	BC	BC'
A'		1	1	1
A	1	1		

$$F_2 = A'B + A'C + AB'$$

PLA: Example...


- PLA program table

	<i>Product Terms</i>	<i>Inputs</i>			<i>Outputs</i>	
		<i>A</i>	<i>B</i>	<i>C</i>	<i>F₁</i>	<i>F₂</i>
A'B	1	0	1	-	-	1
A'C	2	0	-	1	1	1
AB'	3	1	0	-	-	1
B'C'	4	-	0	0	1	-
					T	T
					T/C	

T = in its original form, inverter is blown up
C = in its complement form, inverter is used

PLA: Example...

 - Internal connections of PLA with PLD notation:




Programmable Array Logic (PAL)

- General structure of PAL is very similar to PLA
 - **But**, only difference between these is in a PAL device, only **AND gates are programmable** whereas **OR gates are fixed** by manufacturer.
 - So, PLA is less expensive, **more flexible** and more easier than PAL

Concept of PAL

- External inputs are connected with the AND gates with programmable links
 - Whereas, **the output of AND gates are fed to OR array with fixed connections**
- **All the AND outputs are not fed to all OR gates**
 - Rather, few AND outputs are connected to an OR gate based on the manufacturer's direction (Figure shown)
- Similar **$n \times p \times m$** notation for PAL as PLA:
 - **n** = number of inputs
 - **p** = number of product terms
 - **m** = number of outputs (or sum terms)

PAL: General Structure

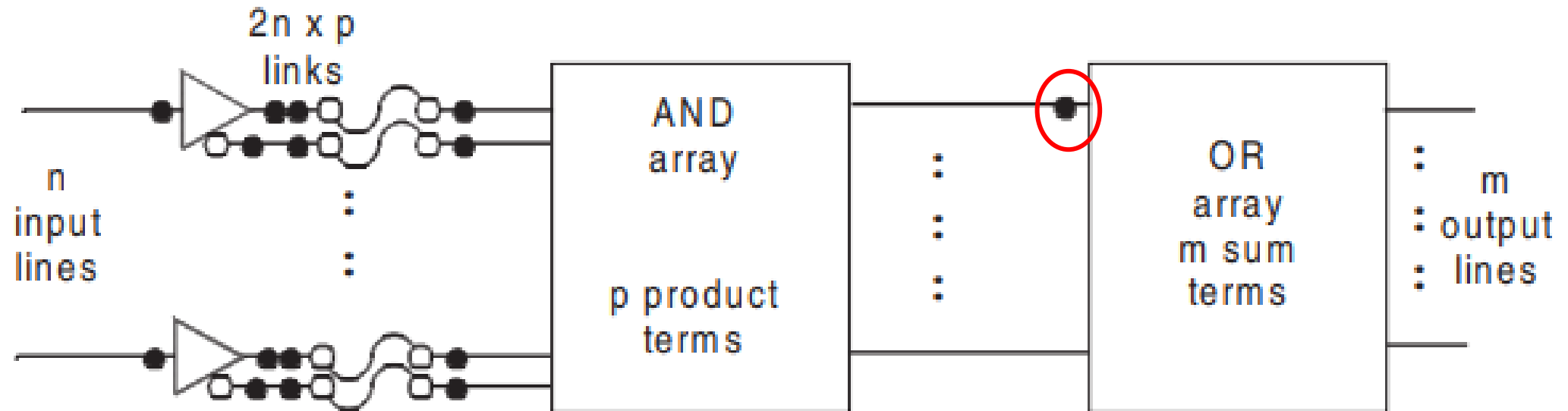



PAL: Example with a 4 x 8 x 3 PAL

Too simple to implement with a PAL

- **Example:** Use a 4 x 8 x 3 PAL to implement the following Boolean expressions

$$F_1(A, B, C) = (1, 2, 4, 5, 7)$$

$$F_2(A, B, C) = (0, 1, 3, 5, 7)$$

- To get required and reduced product terms, **simplified expressions** are:

	B'C'	B'C	BC	BC'
A'		1		1
A	1	1	1	

$$F_1(A, B, C) = AB' + AC + B'C + A'BC'$$

	B'C'	B'C	BC	BC'
A'	1	1	1	
A		1	1	

$$F_2(A, B, C) = C + A'B'$$

PAL: Example with a 4 x 8 x 3 PAL...

- But, in the specified PAL, there is **no** OR gate **with 4 product terms**
 - So alternative realization could be:


$$F_1(A,B,C) = F_3 + B'C + A'BC'$$

$$F_2(A,B,C) = C + A'B'$$

Where $F_3 = AB' + AC$.

- Now these three functions could realize the specified Boolean expressions where F_3 (**sub-function**) has to be inserted as an input to the F_1 again

PAL: Example with a 4 x 8 x 3 PAL...

 




Other PLDs


- Registered PAL devices
 - For **sequential circuits**
- **Generic Array Logic Devices (GAL)**
- **Field Programmable Gate Array (FPGA)**

ALU as Logic Device

 
- ALU is a part of CPU that performs the **calculation** and **condition testing**
 - Considered as fundamental **building block** of CPU



ALU: Example of ALU

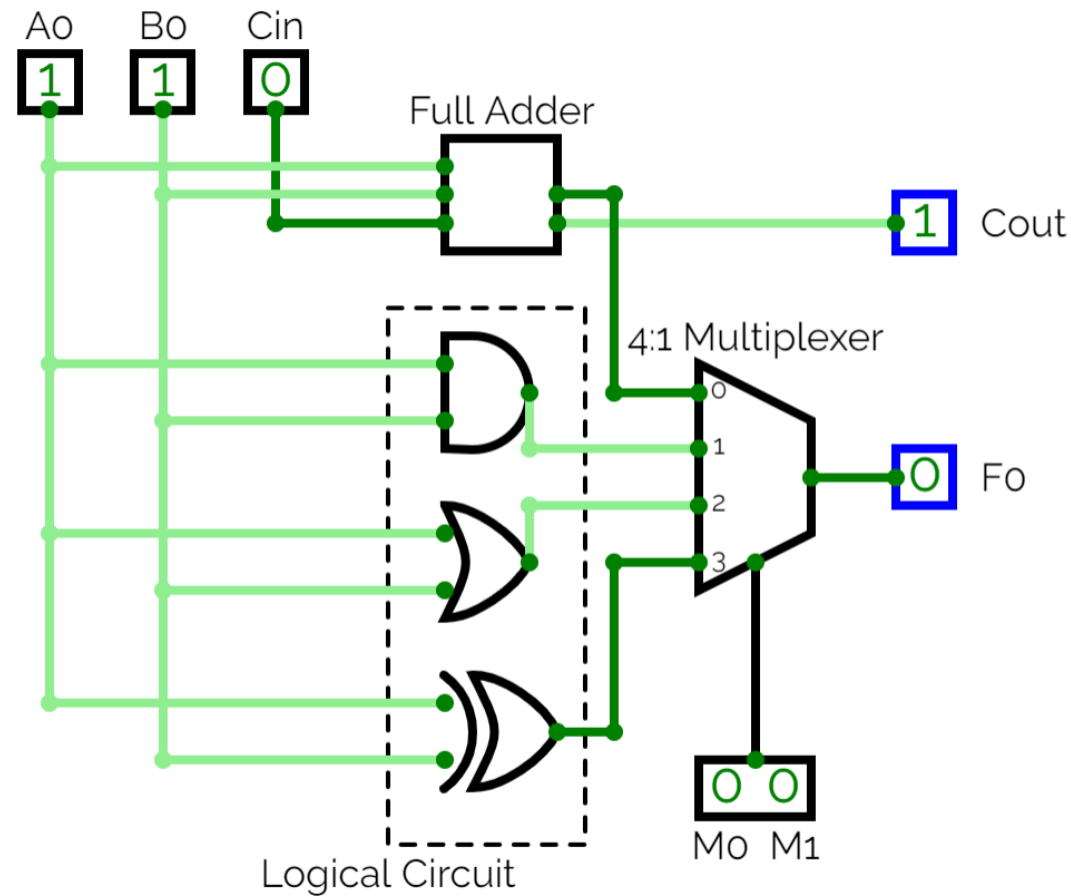

**Circuit Diagram
of 1-bit ALU**

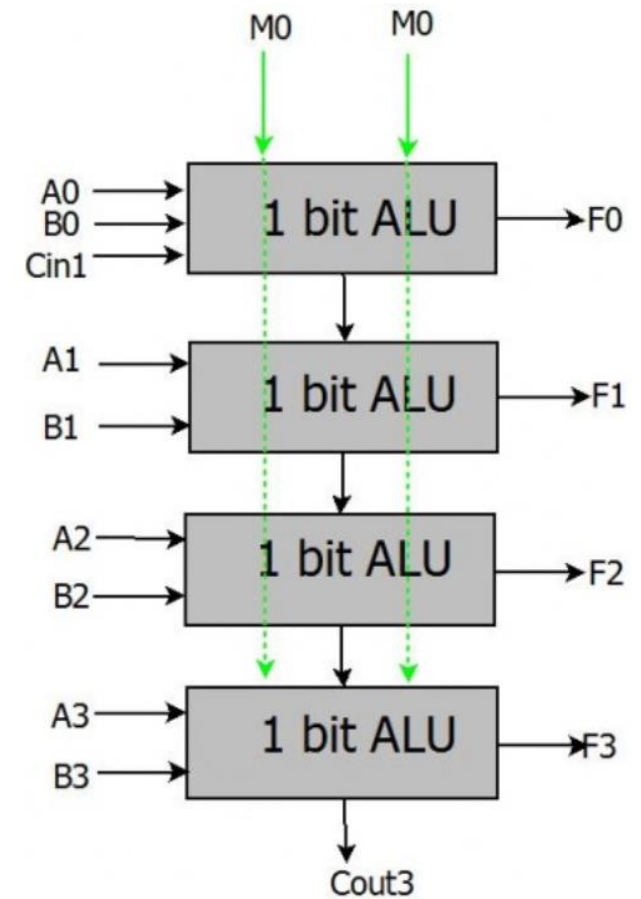

**Block Diagram
of multiple 1-bit ALUs**

ALU: More Complex Example

