



CSE 4205

Digital Logic Design

Register


Course Teacher: Md. Hamjajul Ashmafee

AP, CSE, IUT

Email: ashmafee@iut-dhaka.edu

Introduction

 - A group of **binary cells** that can hold **binary information**
 - Normally, a **group of flip flops** makes a register
 - **n bit register** has **n flip flops** to hold **n bits** of information
- A register may have an **additional combinational circuit** that performs ***data processing*** task





Shift Register: Classification

- **Shift:** Operation to move and store data
- **Direction of shifting**
 - It is capable of shifting its binary contents either to the **right** or to the **left**
- **Types of shifting**
 1. Serial shifting
 2. Parallel shifting





Shift Register: Different Classifications



- **Unidirectional Shift Register**
- **Bidirectional Shift Register**
- **Universal Shift Register**

Shift Register: Basic Types

  1. SISO (IC 74L91)
2. SIPO (IC 74164)
3. PISO (IC 74265)
4. PIPO (IC 74198)



Parallel data outputs

  




Shift Register - SISO


- **Input data** – serially through a single input line
- **Output data** – also serially through a single output line
- **Types** based on direction of shifting
 - Left shift register
 - Right shift register

Shift Register – SISO – Right shift

Circuit Diagram

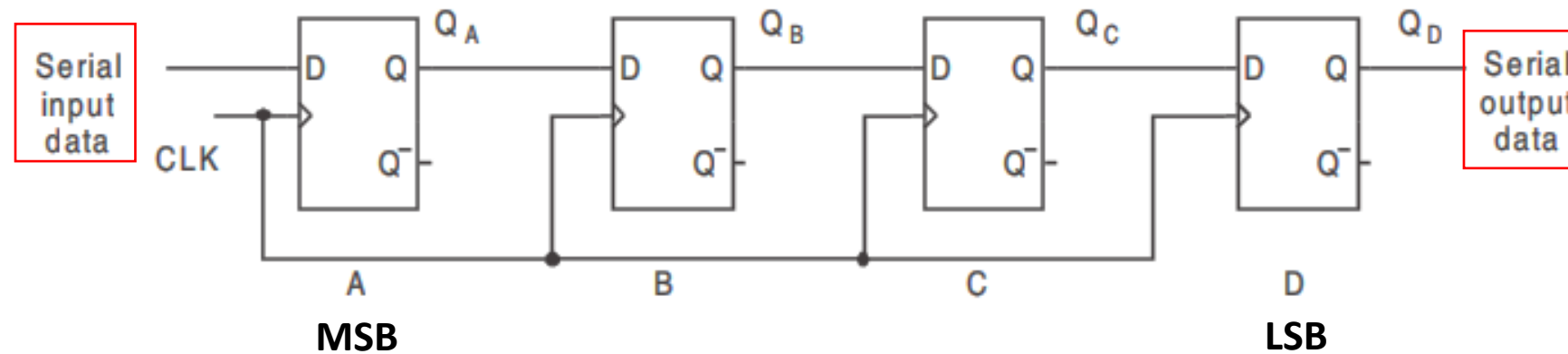


Using D flip flop

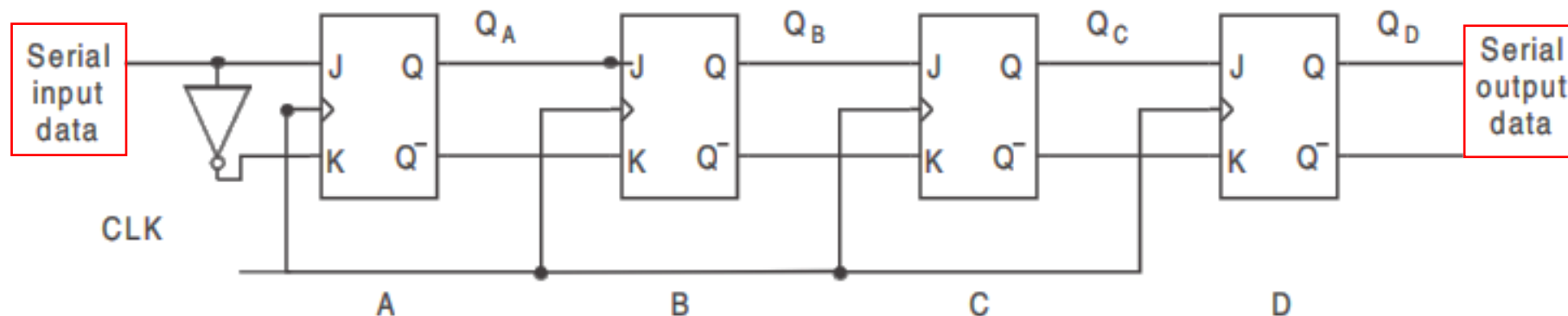


Using JK flip flop

8 Bit SISO Shift Register IC

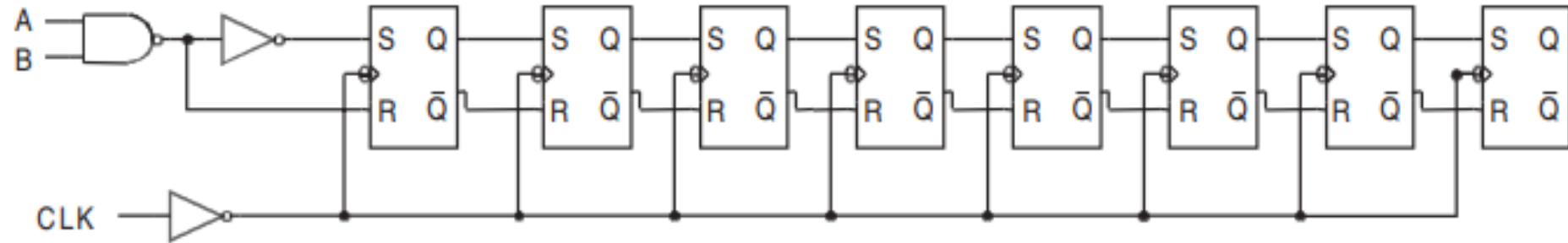

(a) Logic diagram.

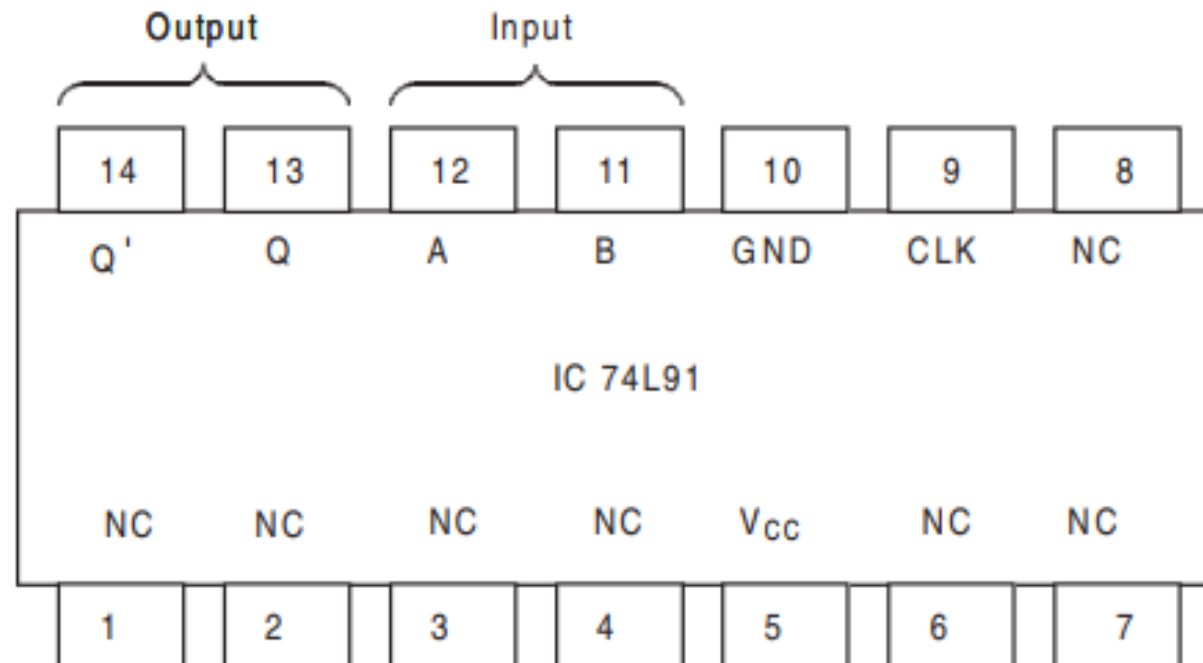

(b) Pinout diagram of IC 74L91.




Shift Register – SIPO


- **Property:** Data is **shifted in serially**, but **shifted out in parallel**
 - All the outputs should be available at the same time by connecting the output of each flip flop to an output pin
 - If the data is stored in the flip flops, **instantly** they are available in the output

8 Bit SIPO Shift Register IC

Outputs

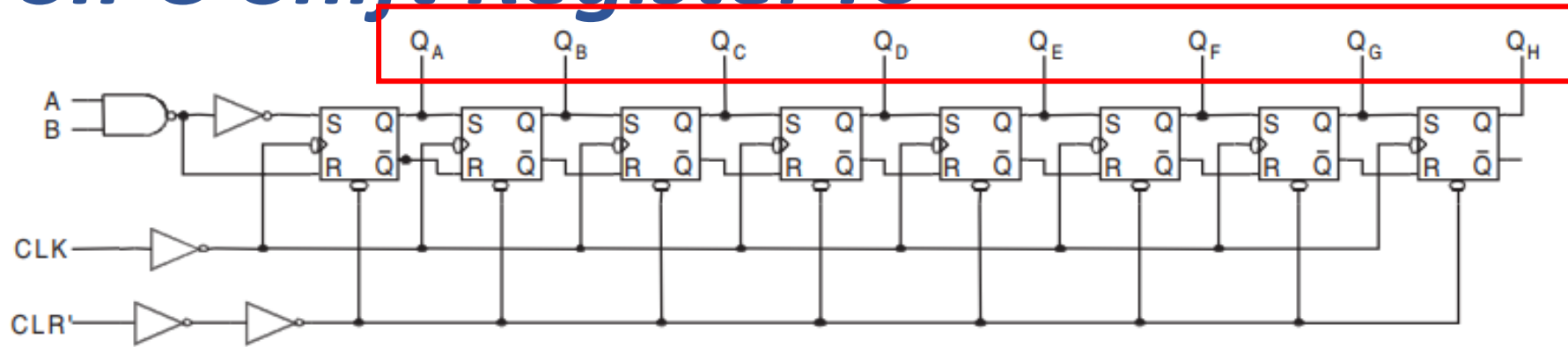

(a) Logic diagram.

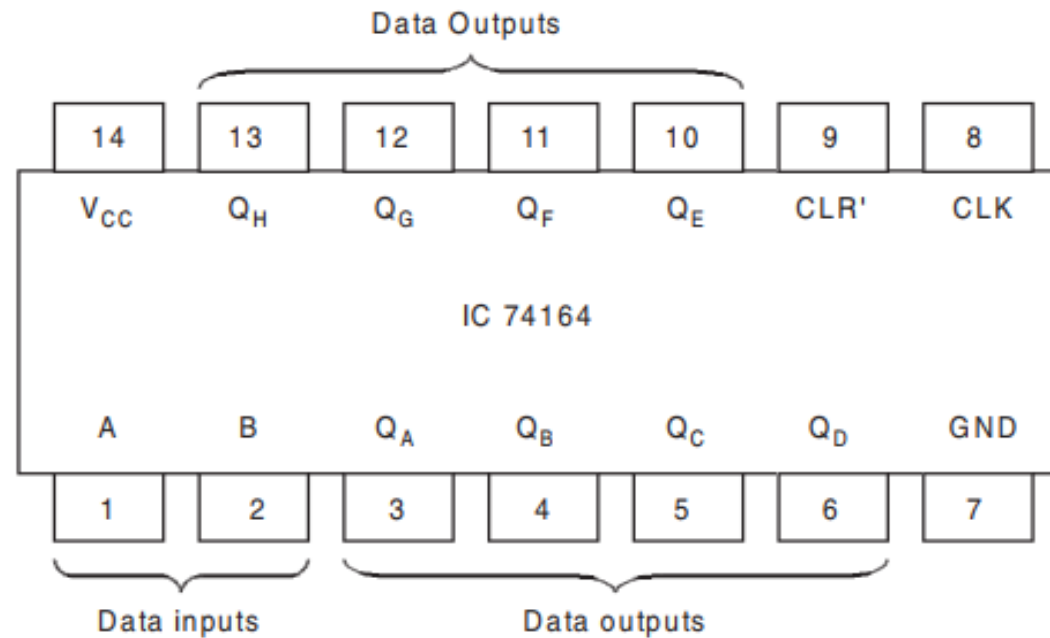

(b) Pinout diagram of IC 74164.




Shift Register – PISO


- **Property:** Data is entered in **parallel manner** into the register
- A **control input (Shift/Load)** is required to allow the all-input data bits **either to enter into** the register in parallel or to **shift out** the data in serial

Shift Register – PISO...


Circuit Diagram

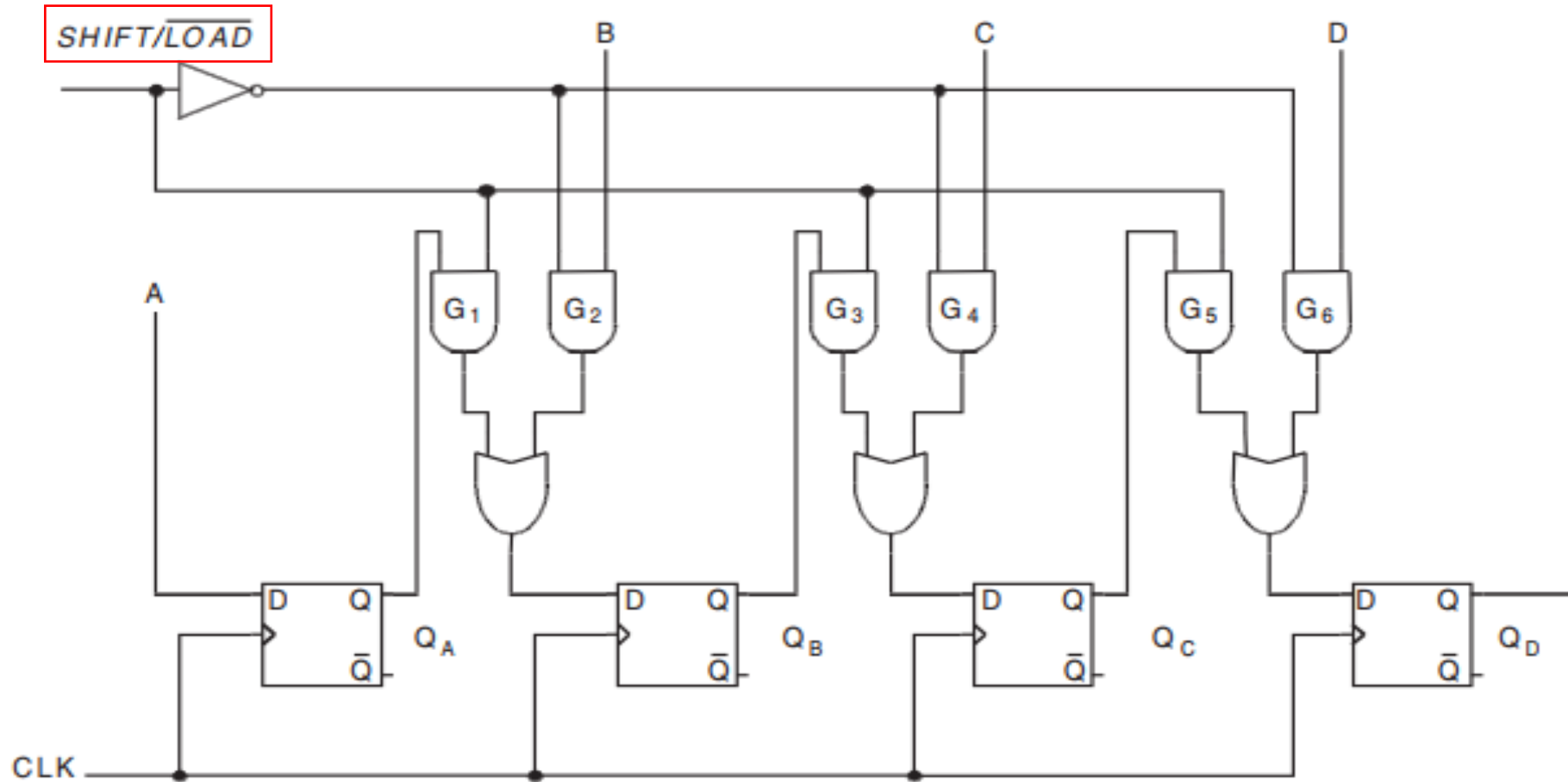

8 Bit PISO Shift Register IC

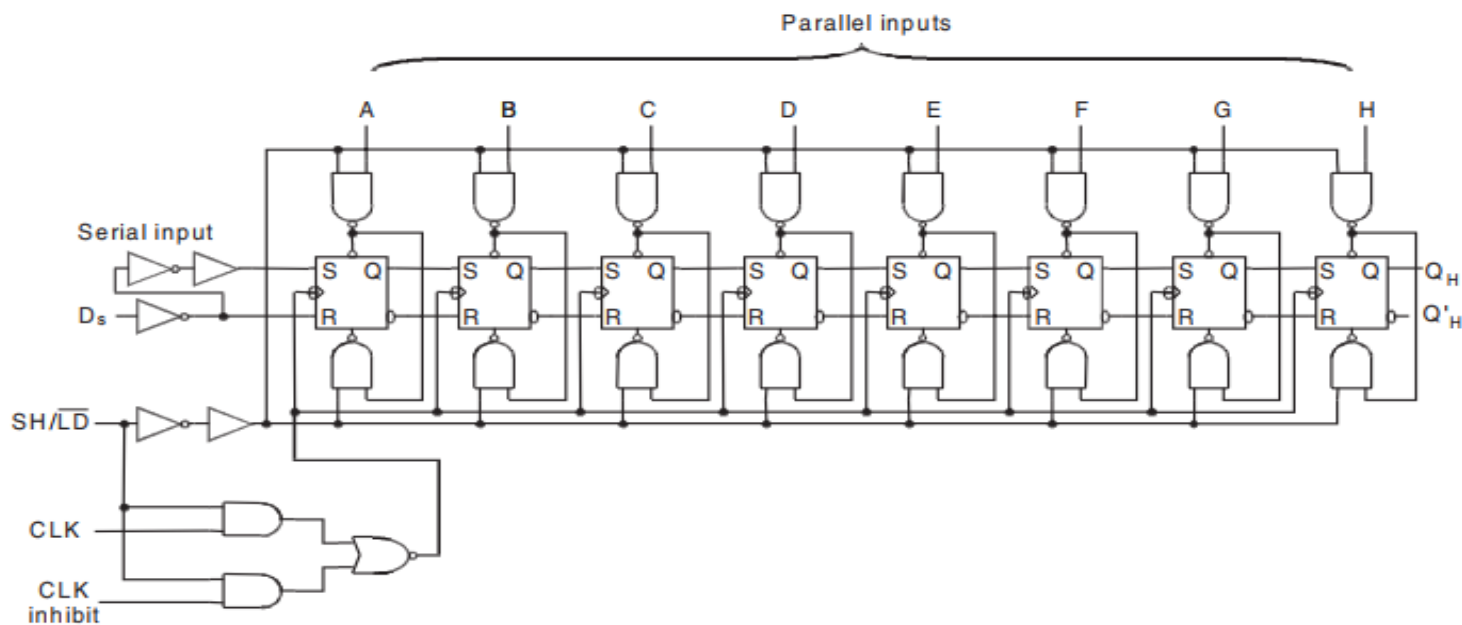

(a) Logic diagram.

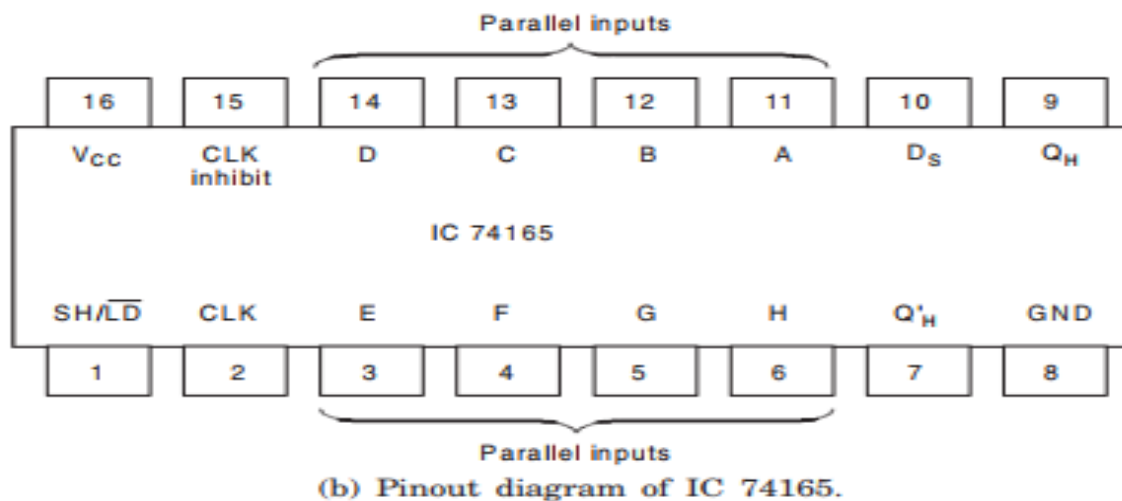




Shift Register – PIPO


- **Property:** Data can be shifted into or out of the register **in parallel**
- **No interconnection** between the flip flops as no serial shift is required

Shift Register – PIPO...

Circuit Diagram

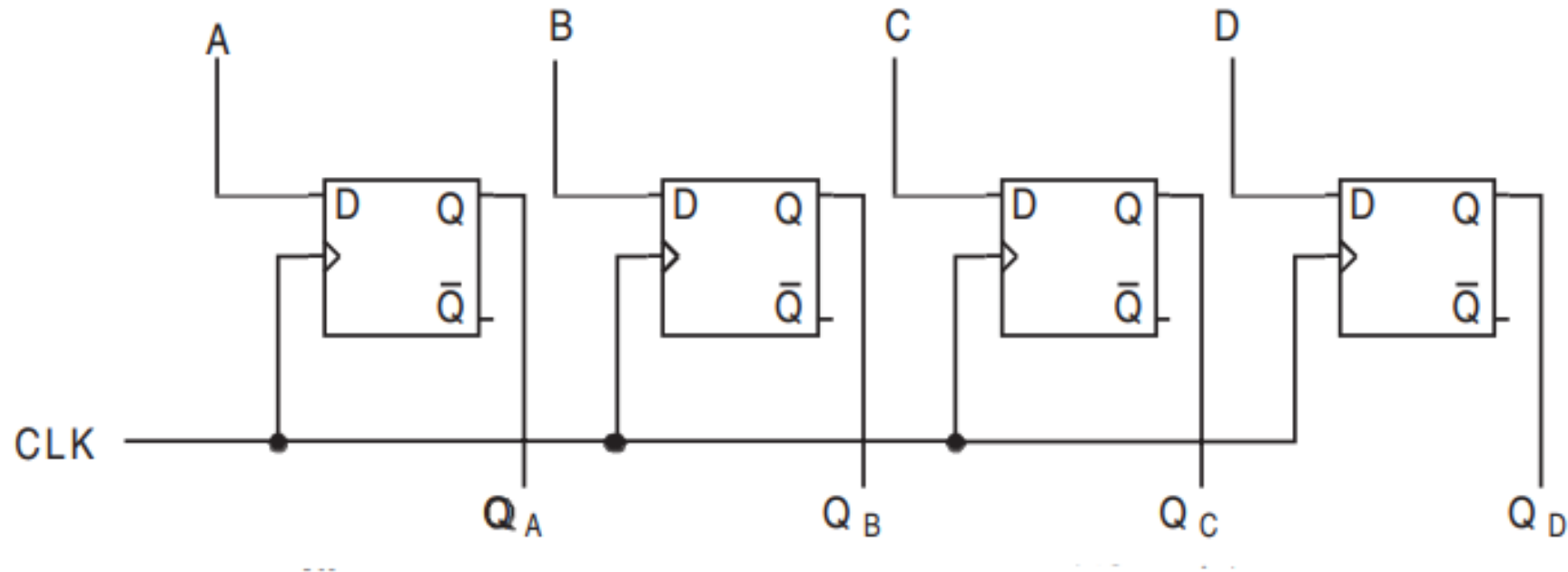

8 Bit PIPO Shift Register IC

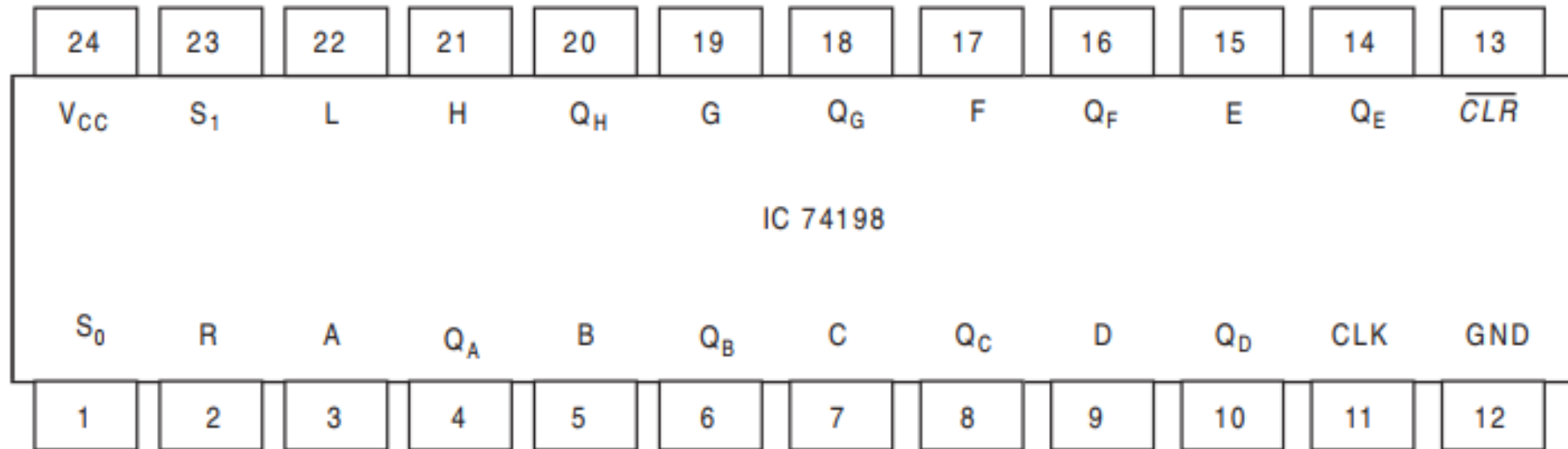






Universal Register


- **Right** or **Left** shift control input
- **Parallel load control**
- **Clear input**
- **Memory state**

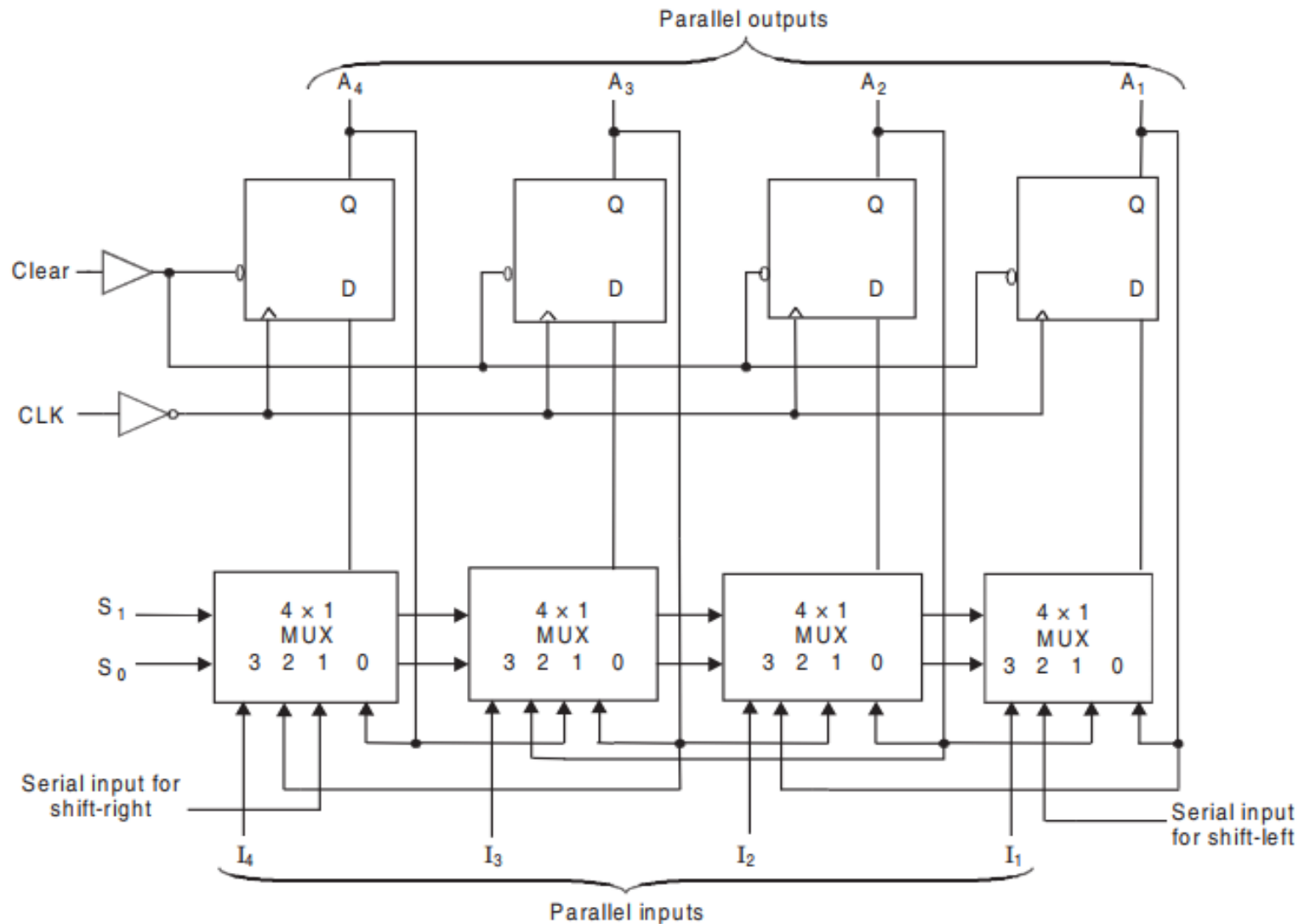4 Bit Universal Register: Circuit Diagram



Mode control		Register operation
S_1	S_0	
0	0	No change
0	1	Shift-right
1	0	Shift-left
1	1	Parallel load

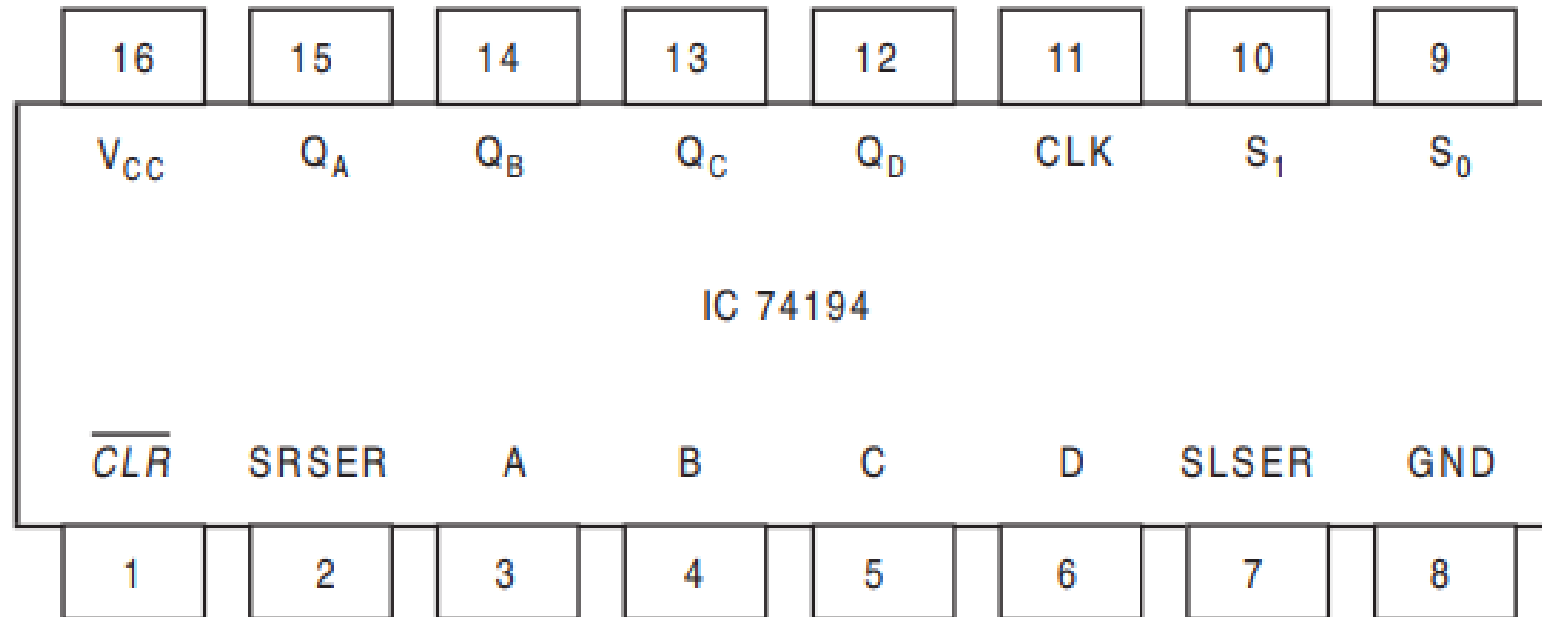4 Bit Universal Register: IC Pinout Diagram





Register used as Counter


- Ring Counter
- Johnson Counter

Ring Counter

- To make a **single** flip-flop “**set state**” once ($Q_i = 1$), while others will be in “**reset/clear state**”
- Output (Q_E) of the last stage is fed back as input (D_A) of the first stage.
- **K-bit** ring counter = **k** different **states**

<i>INIT</i>	<i>CLK</i>	Q_A	Q_B	Q_C	Q_E	<i>State Exp.</i>
L	X	0	0	0	1	X
H	↑	1	0	0	0	Q_A
H	↑	0	1	0	0	Q_B
H	↑	0	0	1	0	Q_C
H	↑	0	0	0	1	Q_E

4 Bit Ring Counter with D Flip Flop

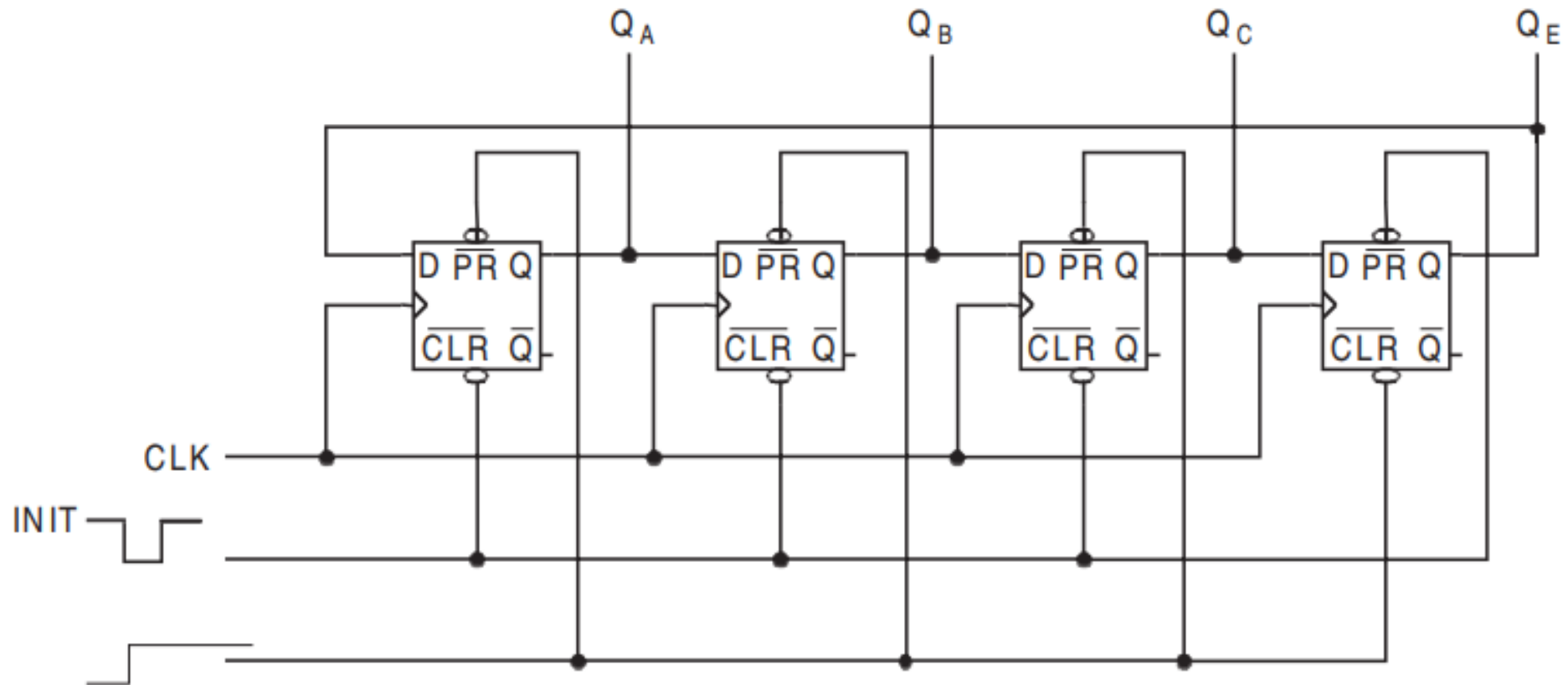




Johnson Counter

- Another shift register counter named as a **switch-tail** ring counter
 - A **circular shift register** where **complemented Output (Q'_E)** of the last stage is fed back as input (D_A) of the first stage.
- For **k-bit** Johnson counter = **2k** different **states**
 - Number of states are **doubled** than **vanilla ring counter**


4 Bit Johnson Counter with D Flip Flop

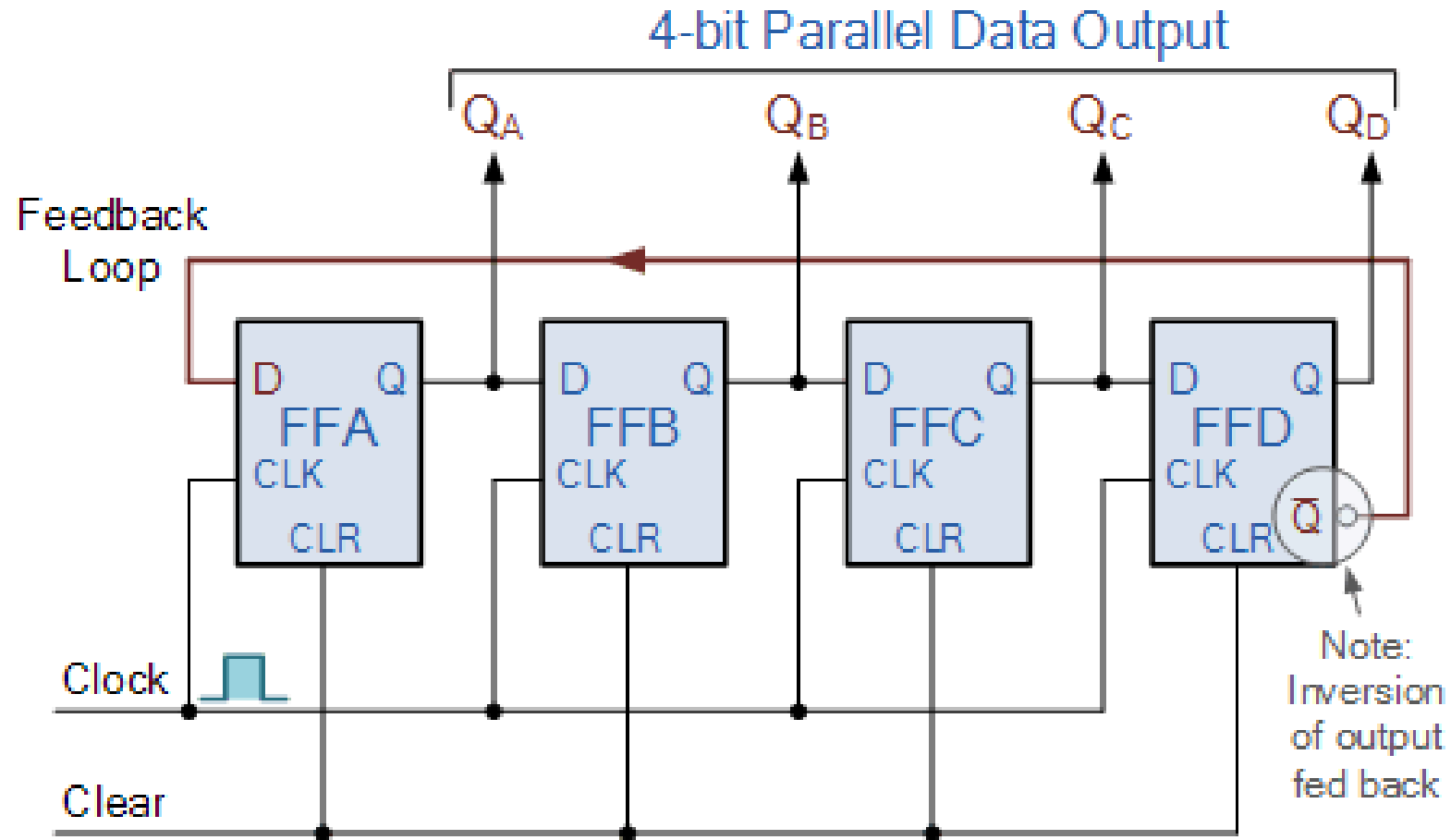

Johnson Counter

Sequence number	Flip-flop outputs				State Exp.
	<i>A</i>	<i>B</i>	<i>C</i>	<i>E</i>	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

 4 Bit Johnson Counter with State Expressions



Johnson Counter: Another Representation

It follows a ***mobius path*** – so known as **mobius counter**






Johnson Counter: Unused States

If Johnson counter enters into any unused state, it will be inside that cycle until it is restarted.


Solution: make a self-correction logic so that it can rectify itself.

Johnson Counter: *Unused States*

 - Used states: 0, 1, 3, 7, 8, 12, 14, 15
- Unused states: 2, 4, 5, 6, 9, 10, 11, 13




Used states' cycle

 

Unused states' cycle

Sequence Generator

- **Definition:**
 - A circuit that generates a **desired sequence** of bits in synchronization with a **clock**
- **Usage:** Random bit generator, code generator, prescribed period generator
- **Construction:** using a **shift register** and **next state decoder**
 - Sequence Output is generated from Q_{n-1} output pin
 - Next state decoder is a function of all present states ($Q_{n-1}, Q_{n-2}, \dots, Q_1, Q_0$)
 - Its output is connected to the input of the shift register (at FF_{n-1})

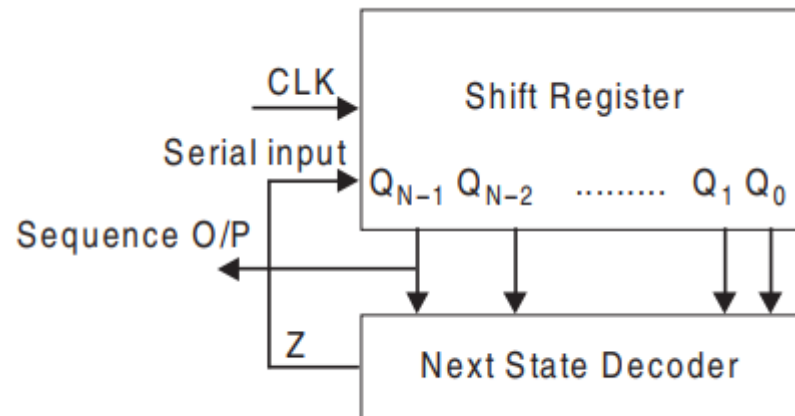

Sequence Generator...

- **Basic concept:**
 - If the length of the pattern = N
 - We could consider a register of n bits where, $n = N$
- But, the challenge is minimize n
- We could start with constraint, **Where, $N \leq 2^n - 1$**

Design a 4-bit Sequence Generator

- Sequence: 1001; sequence length, $N = 4$
- Minimum number of flip-flops n
 - Where, $N \leq 2^n - 1$
 - Here, $n = 3$
- If these three flip-flops doesn't produce all unique states (for inputs), we should increase the number of flip-flops
 - Increment n by 1.

Design a 4-bit Sequence Generator...


CLK	Flip-Flop outputs			Serial Input
	Q_2	Q_1	Q_0	
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1
4	1	0	0	1
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1
4	1	0	0	1

Here, Four states are different by inputs Z.

In the table, Z is true for two times only.

Q_2	$Q_1 Q_0$			
	00	01	11	10
0	X	1	0	X
1	1	X	X	0

$z = Q_1'$

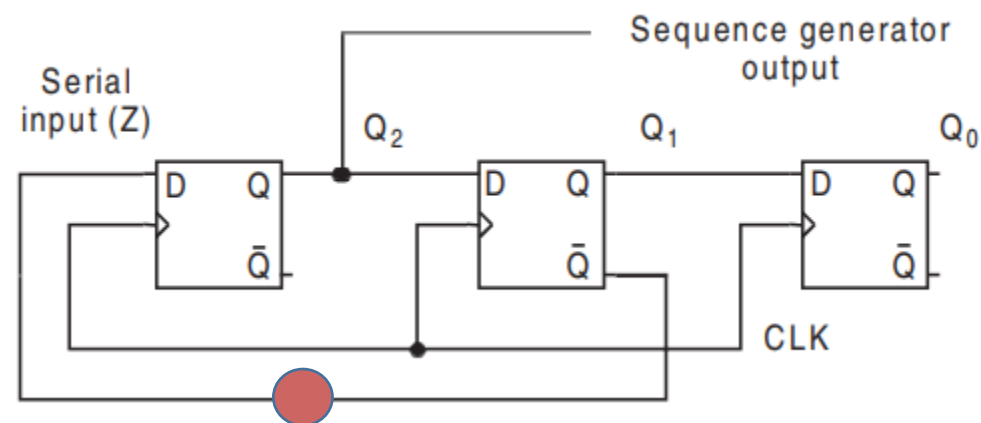

Logic for next state decoder.

Serial Addition

